

**Solution Manual for Electric Machines Principles Applications and
Control Schematics 2nd edition by Dino Zorbas ISBN 1133628516
9781133628514**

Full link download

Solution Manual:

<https://testbankpack.com/p/solution-manual-for-electric-machines-principles-applications-and-control-schematics-2nd-edition-by-dino-zorbas-isbn-1133628516-9781133628514/>

2 Transformers

2.1 Solutions To Exercises

EXERCISE 2-1

$$Z_L = \frac{(120)^2}{5000} = 2.88 \Omega \quad Z_1 = \frac{240 \times 2}{288} = 1.52 \Omega \quad \forall 120\%$$

EXERCISE 2-2

a) $Z_{eH} = 0.5 + j1.2 + (2)^2 (0.125 + j0.30) = \underline{1 + j2.4 \Omega}$

$\frac{1}{4}$

b) $Z_{eL} = 4 (1 + j2.4) = \underline{0.25 + j0.6 \Omega}$

$\frac{5000}{(240)^2}$

c) $Z_{epu} = (0.25 + j0.6) (240)^2 = \underline{0.022 + j0.052 pu}$

d) $V = V_L + I Z$

$$= 1 \angle 0^\circ + 1 \angle -36.9^\circ (0.022 + j0.052) = 1.049 \angle 1.56^\circ$$

$$V_S = 1.049(480) \angle 1.56^\circ = \underline{503.52 \angle 1.56^\circ V}$$

EXERCISE 2-3

$$V_{Z_{pu}} = I_{rpu} Z_{\theta pu}$$

$$= 1.0 Z$$

$$= Z_{epu}$$

EXERCISE 2-4

1. a) Primary:

$$I_L = \frac{1500}{\sqrt{3}(4.16)} = \underline{\underline{208.2 \text{ A}}}$$

$$I_P = 208.2 / \sqrt{3} = \underline{\underline{120.2 \text{ A}}}$$

Secondary:

$$I_P = I_L = \frac{1500}{\sqrt{3}(0.48)} = \underline{\underline{1804.2 \text{ A}}}$$

$$b) \quad Z_{bL} = \frac{(0.48)^2}{1.5} = 0.154 \text{ } \Omega/\text{Phase}$$

$$X_e = 0.06 (0.154) = \underline{\underline{0.0092 \text{ } \Omega/\text{Phase}}}$$

$$Z_{eH} = \frac{(4.16)^2}{1.5} = 11.537 \text{ } \Omega/\text{Phase}$$

$$X_{eH} = 0.06 (11.537) = 0.69 \text{ } \Omega/\text{Phase, star connected}$$

$$= 3 (0.69) = \underline{\underline{2.08 \text{ } \Omega}}, \text{ delta connected}$$

c) Secondary:

$$I_L = I_P = \frac{1500}{\sqrt{3}(0.48)} \cdot \frac{1}{\sqrt{0.06\%}} = \underline{\underline{30.07 \text{ kA}}}$$

Primary:

$$I_L = \frac{1500}{\sqrt{3}(4.16)} \cdot \frac{1}{\sqrt{0.06\%}} = \underline{\underline{3.47 \text{ kA}}}$$

$$I_P = 3.47 \cdot 3 = 2.0 \text{ kA}$$

2. a) Primary

$$I_L = 208.2 (1.333) = \underline{277.6 \text{ A}}$$

$$I_P = 277.6/\sqrt{3} = \underline{160.3 \text{ A}}$$

Secondary:

$$I_L = \frac{2000}{\sqrt{3}(0.48)} = \underline{2405.6 \text{ A}}$$

- b) No change.
c) No change.

EXERCISE 2-5

From

$$\begin{aligned} I_A + I_C &= I_B; & I_C &= I_T \\ I_A \pm I_T - I_S &= 0, & I_B \pm I_T - I_S &= 0 \\ I_T &= \underline{0 \text{ A}}, & I_A = I_B &= \underline{25 \text{ A}} \end{aligned}$$

EXERCISE 2-6

Parameter	$\Delta\text{--}\Delta$	$\Delta\text{--}\text{Y}$
Insulation level of secondary winding	nominal	lower for star winding
Exciting current	non-linear	non-linear
Output voltage waveforms	sinusoidal	sinusoidal

EXERCISE 2-7

c) 120 V coil: $\frac{500}{120} = 4.166 \text{ A}$

240 V coil: 2.08 A

$$\begin{aligned} \text{Load: } S &= \sqrt{3} V_{L-L} I \\ &= \sqrt{3} (0.48) (10.4167) \\ &= \underline{8.66 \text{ kVA}} \end{aligned}$$

EXERCISE 2-8

$$S_b = 500 \text{ kVA} \quad V_b = 480 \text{ V} \quad I_b = \frac{500}{0.48} = 1041.67 \text{ A}$$

$$Z_{e1} = (0.02 + j0.035) \frac{5}{3} = 0.0672 \angle 60.3^\circ \text{ p.u.}$$

$$Z_{e2} = (0.018 + j0.04) \frac{5}{2.5} = 0.0877 \angle 65.8^\circ \text{ p.u.}$$

$$V_1 = V_2$$

$$V_1 = 1 \angle 0^\circ + I_1 Z_{e1}$$

$$V_2 = 1 \angle 0^\circ + I_2 Z_{e2}$$

Thus,

$$I_1 = I_2 \frac{Z_{e2}}{Z_{e1}}$$

$$\begin{aligned} I_1 &= \frac{0.0877 \angle 65.8^\circ}{0.0672 \angle 60.3^\circ} I_2 \\ &= 1.31 \angle 5.5^\circ I_2 \end{aligned}$$

Also

$$I_1 + I_2 = 1 \angle 25.8^\circ$$

or

$$(1.31 \angle 5.5^\circ) I_2 + I_2 = 1 \angle 25.8^\circ$$

From which

$$\begin{aligned} I_2 &= 0.434 \angle 29^\circ \text{ p.u.} \\ &= 0.434 (1041.67) = \underline{452.29 \text{ A}} \end{aligned}$$

and

$$I_1 = 0.567 \angle 23.4^\circ = 0.567 (1041.67) = \underline{590.4 \text{ A}}$$

$$S_2 = 452.29 (0.48) = 217.1 \angle 29^\circ \text{ kVA}$$

$$S_1 = 590.4 (0.48) = \underline{283.4 \angle 23.4^\circ \text{ kVA}}$$

EXERCISE 2-9

Shorting the load will increase by many folds the current through the primary winding of the CT. As a result, the CT will be damaged—if no precaution is taken—due to excessive copper losses. The PT's primary current will remain at its nominal level.

EXERCISE 2-10

- a) PT. When the fuse is blown out the secondary winding becomes open circuited.

There is no danger of fire.

CT. When the fuse is blown out the secondary winding becomes open circuited.

There is a danger of fire.

- b) Voltage and current are phasors while the meters read only scalar quantities.

2.2 Solutions To Problems

PROBLEM 2-1

a) $Z_{eH} = 0.5 + j2.6 + 10^2 (0.005 + j0.026) = 1 + j5.2 \Omega$

$$Z_{eL} = 0.005 + j0.026 + \frac{1}{100} (0.5 + j2.6) = 0.01 + j0.052$$

$$= 0.053 \angle 79.11^\circ \Omega$$

- b) $I_2 = \frac{50000}{(230)} = 217.39 \angle -25.8^\circ \text{ A}$
- $V_L = \angle 0^\circ = 230 \angle -217.39 (0.053) \angle 79.11^\circ \angle 25.8^\circ$
- $\beta = 2.3^\circ, \quad V_L = \underline{222.93 \text{ V}}$

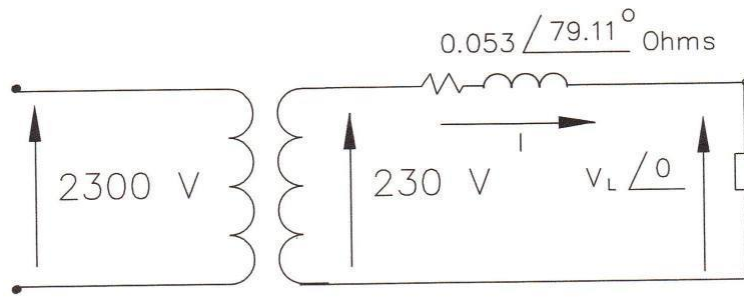


FIG. SP2---1

PROBLEM 2-2

a) $Z_{mH} = \frac{2400}{0.35} = 6857.1 \Omega$

$$R_m = \frac{150}{(0.35)^2} = 1224.49 \Omega$$

$$X_m = \sqrt{6857.1^2 - 1224.49^2} = 6746.93 \Omega$$

$$\underline{Z}_{mH} = 6857.1 \angle 79.7^\circ \angle, \quad \underline{Z}_{mL} = 68.57 \angle 79.71^\circ \angle$$

$$Z_{eL} = \frac{12}{41.67} = 0.288 \Omega, \quad R_{eL} = \frac{320}{(41.67)^2} = 0.184 \Omega$$

$$X_{eL} = (0.288^2 - 0.184^2)^{1/2} = 0.2213 \Omega$$

$$\underline{Z}_{eL} = 0.288 \angle 50.2^\circ$$

$$\underline{Z}_{eH} = 28.8 \angle 50.2^\circ$$

b) $V = 10 (240 + 0.288 \angle 50.2^\circ (41.67 \angle -25.8^\circ))$

$$= 2509.8 \angle 1.1^\circ V$$

$$c) \quad \text{Reg} = \frac{\sqrt{2509.8}}{\# \ 10} \cdot \frac{\% \ 1}{\& \ 240} \cdot (100) = \underline{\underline{4.57\%}}$$

$$! = \frac{10(0.9)}{10(0.9) + 0.320 + 0.15 \sqrt{2509.8\%}^2} = \underline{\underline{0.949}}$$

2400 &

$$d) \quad Z_{B1} = \frac{(240)^2}{10000} = 5.76 \ \Omega$$

$$Z_{epu} = \frac{0.288 \angle 50.2^\circ}{5.76} = 0.05 \angle 50.2^\circ \ \text{pu}$$

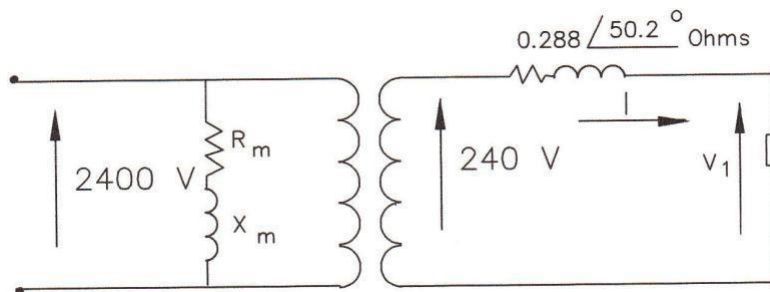


FIG. SP2---2

PROBLEM 2-3

$$a) \quad Z_{B1} = \frac{120^2}{50000} = 0.288 \ \Omega, \quad R_a = 0.023(0.288) = 0.0066 \ \Omega$$

$$I^2 (0.0066) = 600, \quad I = \underline{\underline{300.96 \ A}}$$

$$b) \quad ! = \frac{50}{50 + 0.6 + 0.6} = \underline{\underline{97.66\%}}$$

$$! = \frac{50}{50 + 0.6 + (416.67)^2 (0.0066)} = \underline{\underline{96.6\%}}$$

$$c) \quad Z_e = 0.023 + j0.05 = 0.055 \angle 65.3^\circ \text{ p u}$$

$$V_s = V_L + I Z$$

$$1 \angle 0^\circ = 1 \angle 0^\circ + 1 \angle 0^\circ (0.055 \angle 65.3^\circ)$$

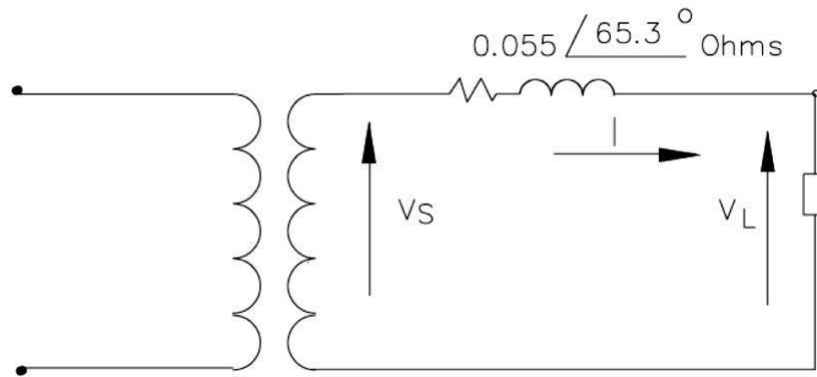


FIG. SP2---3

$$I \angle \mu = I \angle 0^\circ + 0.055 \angle \alpha ; \quad \mu = \Theta + 65.3^\circ$$

$$\cos \beta = 1 + 0.055 \cos \mu$$

$$\sin \beta = 0.055 \sin \mu$$

From the last two relationships

$$\cos^2 \beta + \sin^2 \beta = 1 + (0.055)^2 (\cos^2 \mu + \sin^2 \mu) + 2(0.055) \cos \mu$$

or

$$\cos \mu = - \frac{0.055}{2} = - 0.0275$$

$$\mu = 91.5^\circ$$

and

$$\Theta = 26.3^\circ; \cos \Theta = \underline{0.90 \text{ leading}}$$

PROBLEM 2-4

$$\underline{2.5}$$

$$I \angle 0.9575$$

$$P_z = 100 (100) = 2.5 \text{ kW}, \quad P_m = P_T - P_z = 100,000 - 2500$$

$$P_m = 4438.6 - 2500 = 1938.6 \text{ W}$$

$$1938.6 = K_1 (120)^2 + K_2 \frac{120^3}{60} \quad \dots(1)$$

∇ 60 %

$$1400 = K_1 (100)^2 + K_2 \frac{100^3}{50} \quad \dots(2)$$

∇ 50 %

From (1) and (2),

$$K_1 = 107.75 \times 10^{-3}$$

a) $P_e = 107.75 \times 10^{-3} (120)^2 = \underline{1551.6}$

$P_h = 1938.6 - 1551.6 = \underline{387 \text{ W}}$

b) $P_h = 1400 - 107.75 \times 10^{-3} (100)^2 = \underline{322.5 \text{ W}}$

c) The hysteresis losses will be increased but not substantially.

Original: $P_h = K_2 (60)^2$

New: $P_h = K_2 (50)(2.4)^2$

PROBLEM 2-5

a) 240/120 V

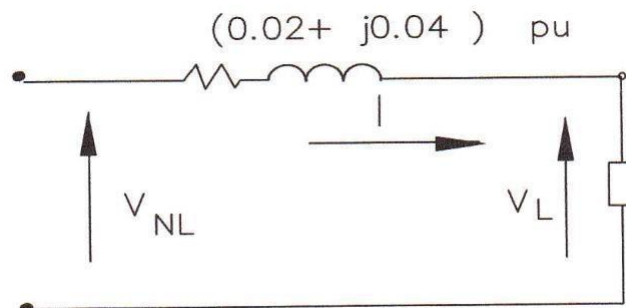


FIG. SP2---5

b) $V_L = V_{nl} - IZ$

$$V_L \angle 0^\circ = 1 \angle 0^\circ - 1 \angle 0^\circ (0.02 + j0.04)$$

$$\beta = 2.3^\circ, V_L = 0.98 \text{ p u}$$

$$\text{Reg} = \frac{1 - 0.98}{0.98} (100) = \underline{\underline{2.04\%}}$$

$$\text{II) } V_L \angle 0^\circ = 1 \angle -1 \angle 36.9^\circ (0.045 \angle 63.4^\circ)$$

$$V_L \angle 0^\circ = 1 \angle -0.045 \angle 100.3^\circ$$

$$\beta = 2.52^\circ, V_L = 1.007 \text{ p.u.}$$

$$\frac{1 - 1.007}{1.007}$$

$$\text{Reg} = \frac{1 - 1.007}{1.007} (100) = \underline{\underline{-0.698\%}}$$

$$\text{III) } V_L \angle 0^\circ = 1 \angle -1 \angle 36.9^\circ (0.045 \angle 63.4^\circ)$$

$$V_L \angle 0^\circ = 1 \angle -0.045 \angle 26.6^\circ$$

$$\beta = 1.1^\circ, V_L = 0.96 \text{ p.u.}$$

$$\text{Reg} = \frac{1 - 0.96}{0.96} (100) = \underline{\underline{4.2\%}}$$

PROBLEM 2-6

$$\text{a) } V_{nl} = 1 \angle 0^\circ + 1.0 \angle 25.8^\circ \times (0.015 + j0.06)$$

$$= 1.0407 \angle 2.6^\circ \text{ p.u.}$$

$$\text{Regulation} = \frac{1.0407 - 1.0}{1.0} (100) = \underline{\underline{4.07\%}}$$

$$P = 0.9 \angle 1 \angle 0.97^\circ = 0.0278 \text{ p.u.}$$

$$\# 0.97 \ \&$$

Actual:

$$P_{cl} = 0.0278 - 0.015 = 0.0128 \text{ p.u.}$$

u X: nominal core loss

$$X (1.0407)^2 = 0.0128$$

$$X = \underline{0.013 \text{ p u}}$$

- b) Set the no-load voltage taps to 1.05 pu

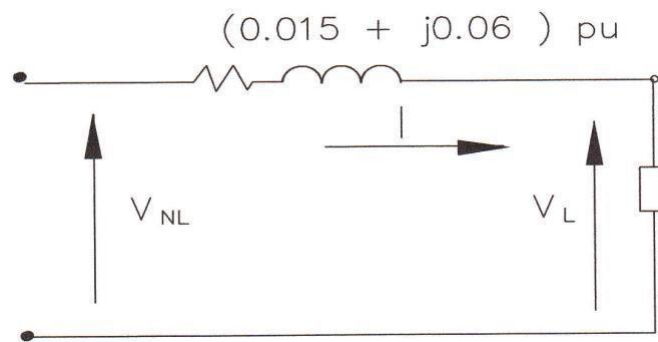


FIG. SP2---6

PROBLEM 2-7

$$\text{a) } I_{AB} = \frac{1480 \text{ } \exists \text{ } 1}{60 \# \sqrt{3} \% 4160} = \underline{4.0 \text{ A}}$$

$$\text{b) } I_{AB} = I_{CB} = \underline{4.0 \text{ A}}$$

$$\text{c) } I_a = \frac{100}{\sqrt{3} (0.48)(0.80)(0.9)} = \underline{167.06 \text{ A}}$$

$$I_{AB} = I_{BC} = I_{CA} = \frac{1480 \text{ } \exists \text{ } 1}{167.06 \# \sqrt{3} \% 4160} = \underline{11.1 \text{ A}}$$

PROBLEM 2-8

$$\text{a) } Z_{bL} = \frac{(0.48)^2}{2} = 0.1152 \text{ } \Omega / \emptyset, \quad Z_{bH} = \frac{(25)^2}{2} = 312.5 \text{ } \Omega / \emptyset$$

$$X_s = \frac{(25)^2 \# 1 \text{ } \exists}{5 + j8} = 0.004 \text{ pu}$$

$\forall 312.5 \%$

$$Z_A = \text{——} = (0.016 + j0.0256) \text{ p u}$$

$$0.005 + j0.01$$

$$Z_B = \frac{0.005 + j0.01}{0.005 + j0.01} = (0.0434 + j0.0867) \text{ pu}$$

$$b) \quad I_1 = \frac{500}{\sqrt{3}(0.48)(0.95)} = 633.1 \angle 36.9^\circ \text{ A}$$

$$I_2 = \frac{600}{\sqrt{3}(0.48)(0.9)(0.9)} = 891 \angle 25.8^\circ \text{ A}$$

$$I_t = I_1 + I_2 = 1517.2 \angle 30.4^\circ \text{ A}$$

$$I_{bL} = \frac{2000}{\sqrt{3}(0.48)} = 2405.6 \text{ A}$$

$$|I_t| = \frac{1517.2}{2405.6} = 0.6307 \text{ pu}$$

$$R_t = 0.016 + 0.01 + 0.0434 = 0.0694 \text{ pu}$$

$$X_t = 0.004 + 0.0256 + 0.062 + 0.0867 = 0.1784$$

$$\begin{aligned} \text{Loss} &= (0.6307)^2(0.0694) = 0.0276 \text{ pu} \\ &= 0.0276 (2000) = \underline{55.2 \text{ kW}} \end{aligned}$$

$$c) \quad V_s = 1 \angle 0^\circ + 0.6307 \angle 30.4^\circ (0.069 + j0.1777)$$

$$= 1 \angle 0^\circ + 0.121 \angle 38.5^\circ ; \quad |V_s| = 1.1 \text{ pu} = \underline{27.4 \text{ kV}}$$

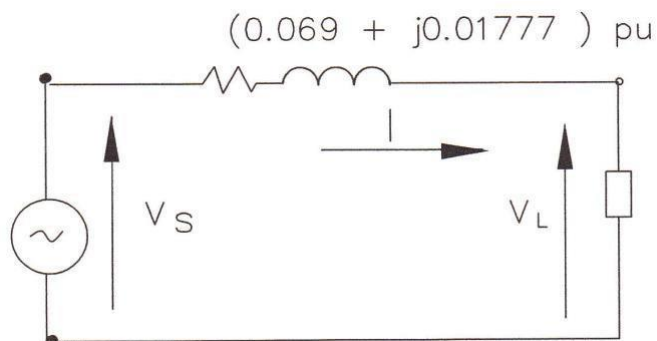


FIG. SP2---8

PROBLEM 2-9

b) The motor current is:

$$I_m = \frac{25}{\sqrt{3}(0.55)(0.8)(0.95)} = 34.53 \text{ A}$$

Take as reference V_{ab} , Phase sequence ABC.

$$I_{m_a} = 34.53 \angle 6.9^\circ \text{ A} \quad I_{m_b}$$

$$= 34.53 \angle 113.1^\circ \text{ A}$$

$$I_{m_c} = 34.53 \angle 126.9^\circ \text{ A}$$

Load P₃

$$I_{ab} = \frac{20}{0.55} \angle 0^\circ = 36.36 \angle 0^\circ \text{ A}$$

Load P₂

$$I_{bn} = \frac{\sqrt{3}}{0.55(0.9)(0.9)} = 38.88 \angle 145.8^\circ \angle 30^\circ = 38.88 \angle 175.8^\circ \text{ A}$$

Load P₁

$$I_{cn} = \frac{\sqrt{3}}{\dots} = 49.72 \angle 53.1^\circ \text{ A}$$

The line currents through the secondary of the transformer are:

$$I_{a-a} = I_{m_a} + I_{ab}$$

$$= 34.53 \angle 6.9^\circ + 36.36 \angle 0^\circ = 70.77 \angle 3.3^\circ \text{ A}$$

$$I_{b-b} = I_{m_b} + I_{bn} - I_{ab}$$

$$= 34.53 \angle 113.1^\circ + 38.88 \angle 175.8^\circ - 36.36 \angle 0^\circ$$

$$= 95.2 \angle 158.7^\circ \text{ A}$$

$$\begin{aligned}
 I_{c-ca} &= I_{mc} + I_{cn} \\
 &= 34.53 \angle 126.9^\circ + 49.72 \angle 53.1^\circ \\
 &= 68 \angle 82.3^\circ \text{ A}
 \end{aligned}$$

Primary of transformer

The per-phase turn's ratio is:

$$\frac{4800}{550\sqrt{3}} = 15.1$$

Then

$$\underline{70.77}$$

$$I_A = 15.1 = \underline{4.68 \text{ A}}$$

$$\underline{95.2}$$

$$I_B = 15.1 = \underline{6.30 \text{ A}}$$

$$\underline{68}$$

$$I_C = 15.1 = \underline{4.5 \text{ A}}$$

- a) The rating of the transformer must be based on the highest winding current requirement.

$$I_{b-b} = 95.2 \text{ A}$$

$$|S| = \sqrt{3} (0.55) (95.2) = \underline{90.70 \text{ kVA}}$$

Use a commercially available transformer whose capacity is

$$3-\emptyset, \quad 4800\text{-}550/317 \text{ V}, \quad 112.5 \text{ kVA}$$

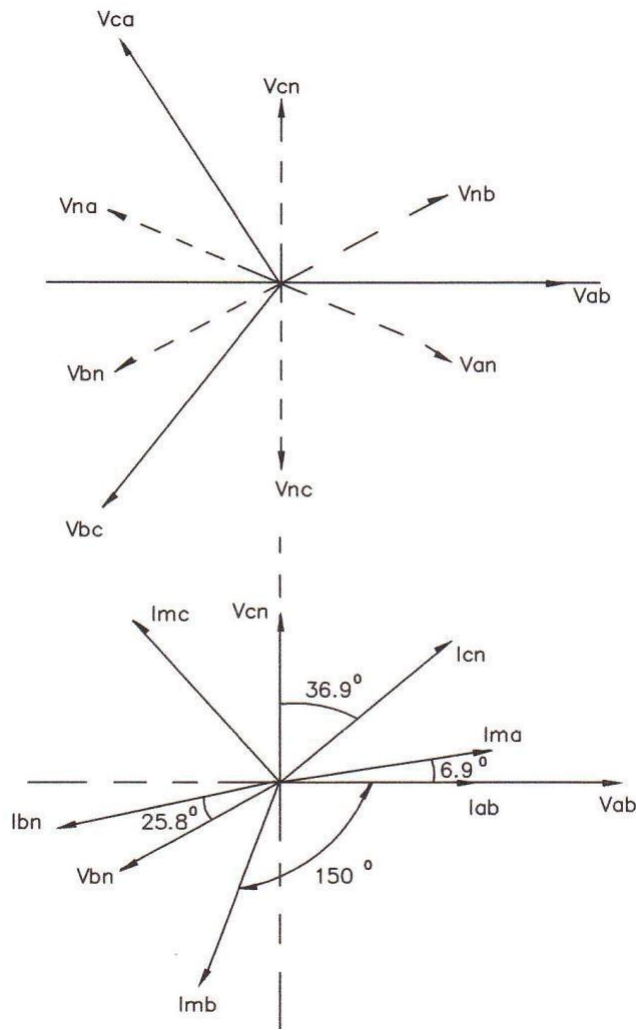


FIG. SP2---9

PROBLEM 2-10

a) $V_1 = 3 I_a + 2 I_b + I_c \quad \dots(1)$

$V_2 = 2 I_a + 3 I_b + I_c \quad \dots(2)$

$V_3 = I_a + I_b + I_c \quad \dots(3)$

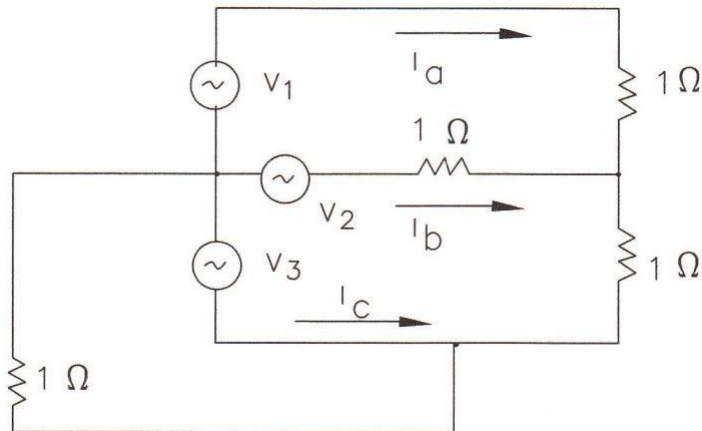


FIG. SP2---10(a)

$$D = \begin{vmatrix} 3 & 2 & 1 \\ 2 & 3 & 1 \\ 1 & 1 & 1 \end{vmatrix} = 3$$

$$N_1 = \begin{vmatrix} V_1 & 2 & 1 \\ V_2 & 3 & 1 \\ V_3 & 1 & 1 \end{vmatrix} = 2V_1 + V_3 - V_2$$

$$= \frac{480}{\sqrt{3}} (2\angle 0^\circ + 1\angle 120^\circ - 1\angle 120^\circ)$$

$$= \frac{480 \times 2}{\sqrt{3}} \text{ V}$$

$$I_a = \frac{N_1}{D} = \frac{480 \times 2}{\sqrt{3} \times 3} = 277.1 \text{ A}$$

Similarly

$$I_b = \frac{480 \times 2}{\sqrt{3} \times 3} \angle 60^\circ$$

$$I_b = 277.1 \angle 60^\circ \text{ A}$$

$$N_3 = \frac{480}{\sqrt{3}} (6) \angle 120^\circ$$

$$I_c = \frac{6480}{3\sqrt{3}} \angle 120^\circ$$

$$= \underline{554.3 \angle 120^\circ \text{ A}}$$

To check

$$V_3 = I_a + I_b + I_c$$

$$= \frac{480}{\sqrt{3}} \angle 120^\circ = 277.1 \angle 0^\circ - 277.1 \angle 60^\circ + 554.3 \angle 120^\circ$$

$$\text{RHS} = \frac{480}{\sqrt{3}} \angle 120^\circ, \quad \text{OK}$$

$V_{mf-g} = 0$, no danger to personnel.

Fuse in phase “c” will blow.

b)

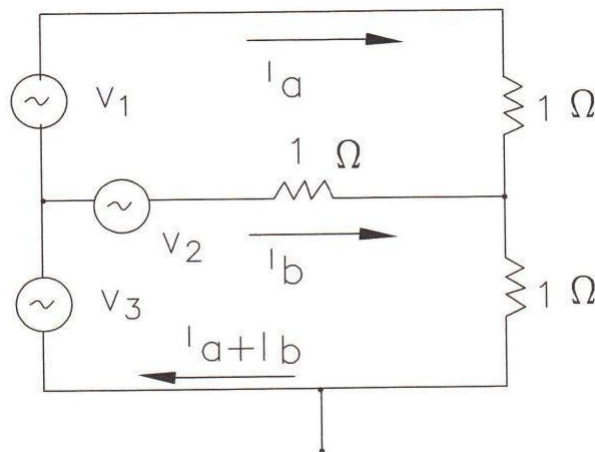


FIG. SP2---10(b)

$$V_1 - I_a - (I_a + I_b) - V_3 = 0 \quad \dots(4)$$

$$V_2 - I_b - (I_a + I_b) - V_3 = 0 \quad \dots(5)$$

From Eqs. (4) and (5):

$$I_a = \frac{1}{\sqrt{3}} [V_2 + V_3 + 2V_1] = \frac{1}{\sqrt{3}} \frac{480}{\sqrt{3}} [1 \angle 120^\circ + 1 \angle 120^\circ + 2 \angle 0^\circ]$$

$$= \frac{277.1}{\sqrt{3}} \text{ A}$$

$I = V - V - 2^{\#}$

$$= \frac{480}{\sqrt{3}} \text{ A}$$

$$= \frac{480}{\sqrt{3}} \text{ A}$$

$$I_c = -(I_b + I_a) = 277.1 (1 \angle 0^\circ + 1 \angle 120^\circ) = 277.1 \angle 120^\circ \text{ A}$$

$$V_{mf-g} = 277.1 \text{ V}$$

Fuses will not blow.

c) $I_c = \infty$

$$V_{mf-g} = 0$$

Fuse in line "c" will blow.

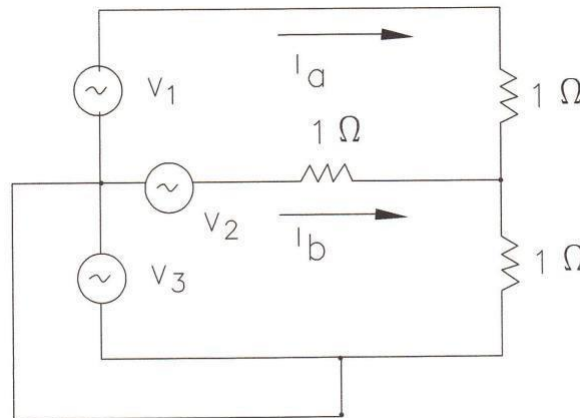


FIG. SP2---10(c)

d) Nominal three-phase operation.

$$V_{mf-g} \approx \underline{277.1 \text{ V}}$$

None of the fuses will blow.

PROBLEM 2-11

- a) $S = 600 (41.67) = \underline{25 \text{ kVA}}$
- b) $25 - 5 = \underline{20 \text{ kVA}}$

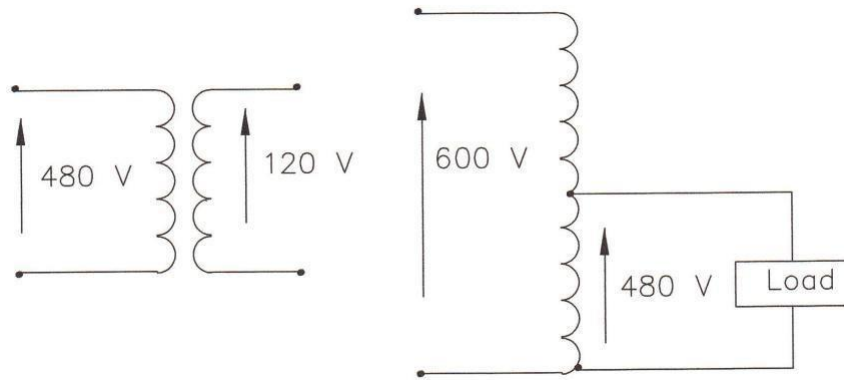


FIG. SP2---11

PROBLEM 2-12

- a) $S = 3.4 (200) = \underline{680 \text{ kVA}}$
 $680 - 200 = 480 \text{ kVA conducted}$

$$\frac{480}{680} (100) = \underline{70.6\%}$$

- b) $P = P_{LT} \left(\frac{1! \nabla}{\nabla} \right) = 200(0.85) \frac{\#}{\exists} \frac{1! 0.96}{0.96 \exists} \& = 7.08 \text{ kW}$

$$\eta = \frac{680 (0.85)}{680 (0.85) + 7.08} = \underline{0.99}$$

- c) $Z_b = (0.02 + j0.06)5 = \underline{\underline{10.75 \text{ kA}}}$

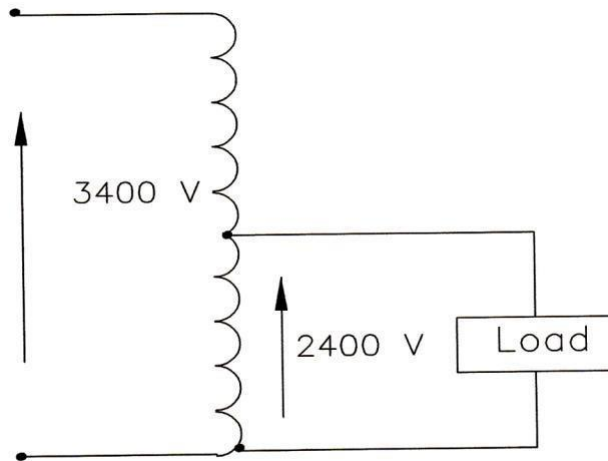


FIG. SP2---12

PROBLEM 2-13

$$S_b = 1000 \text{ kVA} \qquad V_b = 480 \text{ V} \qquad I_b = \frac{1000}{480} = 2.08 \text{ kA}$$

$$T-1 \quad Z_{e1} = (0.02 + j0.04) \frac{1000}{550} = 0.0364 + j0.0727 = 0.0813 \angle 63.4^\circ \Omega$$

$$T-2 \quad Z_{e2} = (0.02 + j0.05) \frac{1000 \times 468^2}{550 \times 480^2} = 0.0346 + j0.0864 = 0.0931 \angle 68.2^\circ \Omega$$

$$\frac{V_1}{480}$$

$$V_2 = 468 = 1.0256$$

$$V_1 \angle 0^\circ = 1 \angle 0^\circ + I_1 Z_{e1} \qquad \dots(1)$$

$$V_2 \angle 0^\circ = 1 \angle 0^\circ + I_2 Z_{e2} \qquad \dots(2)$$

$$\frac{V_1}{480} = 1.0256 = \frac{1 \angle 0^\circ + I_1 Z_{e1}}{480} \qquad \dots(3)$$

$$V_2 = 468 = 1 \angle 0^\circ + I_2 Z_{e2}$$

$$I = I_1 + I_2 \qquad \dots(4)$$

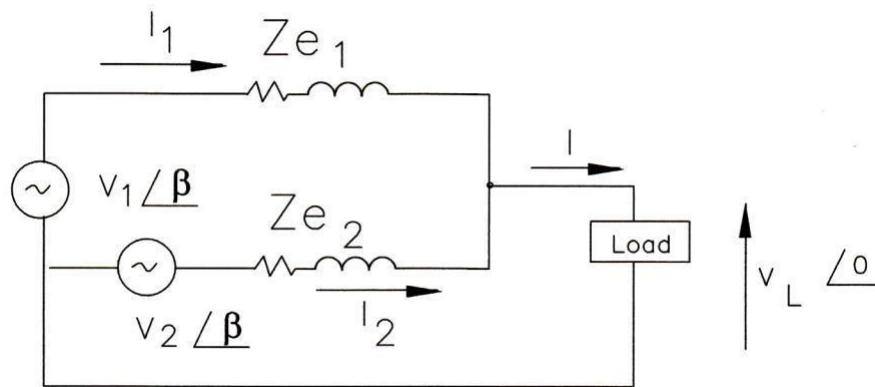


FIG. SP2---13

From (3) and (4)

$$I_1 = 0.655 \angle 32.2^\circ \text{ p.u.}$$

$$I_2 = 0.36 \angle 14^\circ \text{ p.u.}$$

a) $V_1 \angle = 1 \angle 0^\circ + 0.655 \angle 32.2^\circ (0.0813 \angle 63.4^\circ)$

$$= 1.0455 + j0.0276 = 1.0459 \angle 1.5^\circ$$

$$= 1.0459 (4160) = \underline{4350.8 \text{ V, L-L}}$$

b) $T-1I_1 = 0.655(2.08) = \underline{1.36 \text{ kA}}$

$$T-2I_2 = 0.36(2.08) = \underline{750 \text{ A}}$$

c) $T-1S_1 = 0.655 (1) [1000] = \underline{655 \text{ kVA}}$

$$T-2S_2 = 0.36 (1000) = \underline{360 \text{ kVA}}$$

$$\frac{V_1}{V_2} = \frac{1.0459}{1.0198}$$

d) $V_2 = 1.0256 = 1.0256 = 1.0198$

$$I = \frac{V_1}{Z_1 + Z_2} = \frac{1.0459 \angle 1.5^\circ}{0.0364 + 0.0346 + j(0.0727 + 0.0864)} = \frac{1.0459 \angle 1.5^\circ}{0.071 + j0.1591}$$

$$\begin{aligned}
 &= 0.0261 + j0.0007 = 0.0261 \angle 1.5^\circ \\
 &\quad \frac{()0.1742 \angle 66^\circ}{} \\
 &= 0.1498 \angle 64.5^\circ \\
 &= 0.1498 (2.08) = \underline{312 \text{ A}}
 \end{aligned}$$

$$\begin{aligned}
 &= + = 1.0459 \angle 1.5^\circ + 1.0198 \angle 1.5^\circ \\
 \text{e) } I_1 I_2 &= \frac{1.0459 \angle 1.5^\circ}{0.0813 \angle 63.4^\circ} \frac{1.0198 \angle 1.5^\circ}{0.0931 \angle 68.2^\circ} \\
 &= 12.8647 \angle 61.9^\circ + 10.9538 \angle 66.7^\circ \\
 &= 10.3922 \angle 21.4088^\circ = 23.799 \angle 64.1^\circ \\
 &= 23.799 (138.8) = \underline{3.3 \text{ kA}}
 \end{aligned}$$

PROBLEM 2-14

$$\text{a) } (1) Z_{bH} = \frac{(25)^2}{1} = 625 \Omega/\emptyset$$

$$20 + j30$$

$$Z_f = \frac{1}{625} = (0.032 + j0.048) \text{ p u}$$

$$Z_t = 0.032 + j0.048 + j0.06 = 0.032 + j0.108 = 0.1126 \angle 73.5^\circ \text{ p u}$$

$$V_L = 1 \angle 0^\circ = 1 \angle -0.1126 \angle 73.5^\circ (1 \angle 25.8^\circ)$$

$$\beta = 4.77^\circ, V_L = 0.92 \text{ p u } V_L$$

$$= \underline{441.9 \text{ V, L-L}}$$

$$I = \frac{1000}{\sqrt{3}(0.48)} = \underline{1202.8 \text{ A}}$$

$$I_m = 1202.8 \# \frac{5 \text{ } \exists}{\text{---}} \& = \underline{4 \text{ A}}$$

$$\forall 1500 \%$$

$$(2) I = \frac{1}{0.1126} = 8.88 \text{ p u}$$

$$I = 0.88 (1202.8) = \underline{10.7 \text{ kA}}$$

$$I_m = 10.7 \# \frac{5 \text{ } \exists}{\text{---}} \& = \underline{35.6 \text{ A}}, \quad V = 0 \text{ Volts}$$

$$\forall 1.5\%$$

$$(3) X_s = \frac{(25)^2}{500} = 1.25 \Omega/\emptyset \quad X_{spu} = \frac{1.25}{625} = 0.002 \text{ p u}$$

$$X_t = 0.002 + 0.048 + 0.06 = 0.11$$

$$V_L = 1 \angle 0^\circ = 1 \angle -1.0 \angle 25.84^\circ (0.032 + j0.11)$$

$$\beta = 6.5^\circ, \quad V_L = 1.02 \text{ pu}, \quad V_L = \underline{489.2 \text{ V}}$$

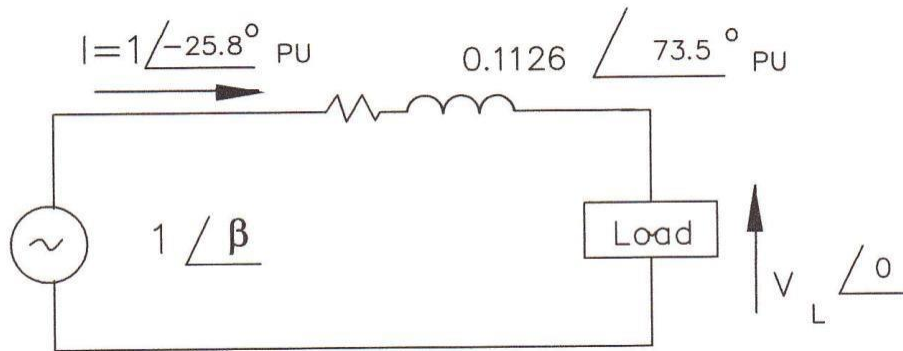


FIG. SP2---14

PROBLEM 2-15

$$\text{Factor: } r_x (1 + r_x)^n = \frac{(1 + r_x)^n - 1}{r_x} = \frac{(1 + 0.0185)^5 - 1}{0.0185} = 1.1$$

$$= 4.77338 \qquad = 1.0185 - 1$$

$$= 0.0185$$

Note: In some publications the exponent n in the denominator is replaced by n!

∇ 1%
2&

a) Manufacturer (A):

$$! 3E^2$$

Losses 3 + #

$$\frac{\& (12) = 9.75 \text{ kW}}{\nabla 4 \%}$$

$$A = 9.75 (365)(24)(0.06) = \$5124.6$$

$$P = 5124.6 (4.7338) = \$24,258.8$$

$$P_T = 30000 + 24258.8 = \underline{\$54,259}$$

Manufacturer (B):

$$\text{Losses } 2.5 + \# \frac{! 3 \exists^2}{\forall 4 \%} \& 9.5 = 7.8438 \text{ kW}$$

$$A = 7.8438 (365)(24)(0.06) = \$4122.675$$

$$P = 4122.675 (4.7338) = \$19,515.9$$

$$P_T = 35000 + 19515.9 = \underline{\underline{\$54,516}}$$

b) Similarly,

Manufacturer (A): \$44,928

Manufacturer (B): \$47,129

c) Manufacturer (A): \$48,660

Manufacturer (B): \$49,928

PROBLEM 2-16

The rms value (I) of the line current is

$$I = \sqrt{\frac{! 10 \exists^2}{\forall 2 \%} + \frac{! 30 \exists^2}{\forall 2 \%} + \frac{! 15 \exists^2}{\forall 2 \%} + \frac{! 10 \exists^2}{\forall 2 \%}} = 74.9166 \text{ A}$$

The per unit values of the component line current are

$$I_1 = \frac{! 10 \sqrt{2} \exists}{\forall 74.9166 \%} \& = 0.9439$$

$$I_3 = \frac{! 30 \sqrt{2} \exists}{\forall 74.9166 \%} \& = 0.2832$$

$$I_5 = \frac{! 15 \sqrt{2} \exists}{\forall 74.9166 \%} \& = 0.1416$$

$$I_7 = \frac{10\sqrt{2}}{74.9166} = 0.0944$$

and

$$k = (0.9439)(1)^2 + [(0.2832 \times 3)^2 + (0.1416 \times 5)^2 + (0.0944 \times 7)^2]$$

$$= \underline{2.55}$$

A k-4 type of transformer is required.