

Solution Manual for Analog Circuit Design Discrete and Integrated 1st Edition Franco 0078028191 9780078028199

Full link download

Solution Manual: <https://testbankpack.com/p/solution-manual-for-analog-circuit-design-discrete-and-integrated-1st-edition-franco-0078028191-9780078028199/>

<https://testbankpack.com/p/solution-manual-for-analog-circuit-design-discrete-and-integrated-1st-edition-franco-0078028191-9780078028199/>

2.1 Two conditions are necessary for successful BJT operation: (a) the emitter must be doped much more heavily than the base; (b) the emitter and collector must be separated by a thin contiguous base.

In the case of two discrete diodes, it is not known a priori whether (a) is met; (b) is certainly not met, as the two anodes are not contiguous; the holes injected from the emitter-acting anode would rather recombine with the electrons supplied by the "base" wire, than progress towards the collector-acting anode.

In the case of two half-BJTs, condition (a) is met, but condition (b) still isn't, as the two base regions, though thin, are not contiguous, but separated by interconnecting wires. The electrons supplied by those wires will recombine with the holes injected by the emitter, resulting in virtually zero collector current. Thus,  $\beta_F \cong I_C/I_B = 0$ .

2.2

$$(a) I_s = 10 \times 20 \times 10^{-8} \frac{1}{10^{-4}} 2 \times 10^{20} \frac{1}{100} \times \frac{1}{510} \approx 7.8 \text{ A}$$

$$\beta_F = \frac{1}{\frac{1}{100} + \frac{1}{510}} = 351$$

$$(b) 1 - 0.16 \approx 0.84 \text{ A}$$

$$I_e = I_c / \beta_F = 0.84 / 351 = 2.4 \text{ A}$$



$$(c) I_c = 0.84 \text{ A} = 840 \text{ mA} = 0.84 \text{ A}$$

[23] @)  $pe - so(h+)y - 0, - \beta Vee$

$$I, \quad / \quad / \quad + \quad \Lambda - 250 = 50$$

$$\frac{500}{2} \frac{W?}{201506L} \Rightarrow Wg - 10 \gg$$
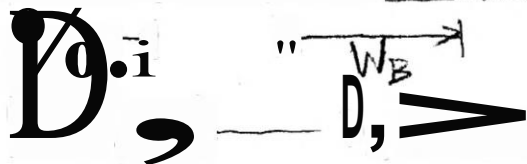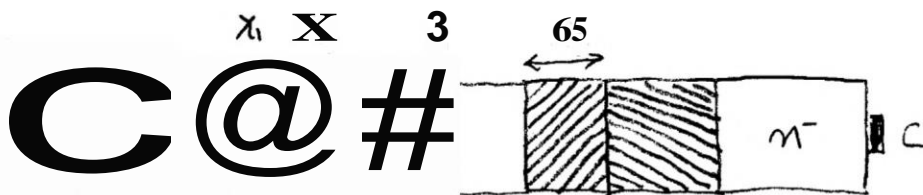
$$\frac{L}{500}, \frac{Pe}{\beta Vee W} \gg \frac{1811 \cdot @4 ti's}{18 \times 10^6 We} We - 0.520 a.$$



$$h.6 \frac{10^4}{2} F \gg, \quad \} = 700 \gg v$$

$$\frac{108}{1GT, jot? 1j7no?} \gg m$$

$$\chi - \#it?e. - "A = a \ll$$

$$\chi_{30} = \sqrt{\frac{2 \times 10^{-12} \times 0.7}{1.6 \times 10^{-19} \times 10^{17}} \frac{10^{15}}{10^{17} + 10^{15}}} = 9.4 \text{ mm}$$

$$D_1 = W_E + \chi_1 = 520 \text{ mm} + (1.1 \text{ mm}) \sqrt{1 - \frac{0.7}{0.94}} \approx 520 \text{ mm.}$$

$$D_2 = W_B + \chi_2 + \chi_3 = 1,039 \text{ mm} + (108 \text{ mm}) \sqrt{1 - \frac{0.7}{0.94}} + (9.4 \text{ mm}) \sqrt{1 - \frac{0.7}{0.94}} \approx 1,039 + 55 + 18 = 1,112 \text{ mm.}$$

2.4

$$(a) I_s = (25 \times 10^{-4})(50 \times 10^{-4}) \frac{1}{10^{-4}} \times 2 \times 10^{20} \frac{1.6 \times 10^{-19}}{10^{17}} 8 = 0.32 \text{ fA.}$$

$$\beta_F = \frac{1}{\frac{3}{8} \frac{10^{17}}{10^{19}} \frac{1}{1} + \frac{(10^{-4})^2}{2 \times 100 \times 10^{-9} \times 8}} = \frac{1}{\frac{1}{267} + \frac{1}{160}} = 100$$

$$(b) I_s = \frac{K_1}{W_B} \Rightarrow I_s \text{ doubles to } 0.64 \text{ fA.}$$

$$\beta_F = \frac{1}{K_2 W_B + K_3 W_B^2} \Rightarrow \beta_F = \frac{1}{\frac{0.5}{267} + \frac{0.5^2}{160}} = \frac{1}{\frac{1}{533} + \frac{1}{640}} = 291.$$

$$(c) I_s = 0.32 \text{ fA (unchanged).}$$

$$\beta_F = \frac{1}{K_3/W_E + 1/160} = \frac{1}{\frac{1}{267 \times 2} + \frac{1}{160}} = 123.$$

$W_B$  affects both  $I_s$  and  $\beta_F$ , and halving it will double  $I_s$  and increase  $\beta_F$  by more than a factor of 2.

$W_E$  affects only  $\beta_F$ , and doubling it will halve the B-E diffusion component of  $I_B$ , thus increasing  $\beta_F$ .

$$5] @ 1e - 10 - A, V_e = 0.04 - \frac{40}{40.15} - 0.002 \text{ V}$$

$$e - 4 = 1.00 \text{ sA}$$


$$+ \frac{1}{7n_0 \sqrt{u_{717}}} \approx \frac{.095}{7871} \approx \xi/4$$

$$T_{cle-le} = 100.5 - 0.00 \text{ V} = 99 \text{ A.}$$


$$(1) I_{es} = 10. \text{ V } 2; T_{seA}.$$

$$(2) Z_c = 0, 1\% - IE \text{ e/k}$$



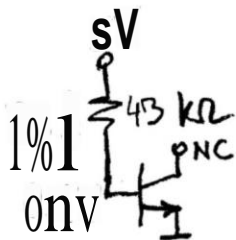

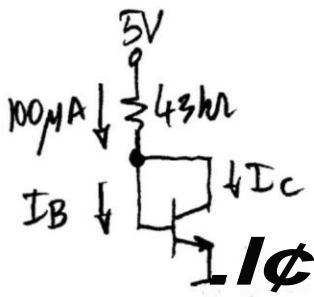$I = 7, -00h = e. = 0$   
 $b_{eh} \approx A$ ,  $-He \rightarrow P$   
 $0.1 \mu A$  tied to  $Z_{po} \gg g$   
 $0.1 \mu A$



$1e-100nA$  ( $0Ah$ ,  $ho \tau 6$ ,  
 $nl \ll 1A$   $Iodeho \ 6t. \langle \rangle$ )  
 $Tc + J = 100E + V = 100A$   
 $> 7 nA$  ( $\%00\{so \ BE + ho$   
 $\%80\}$ , recombining » ai  $d e \&.ans \ rt \gg ?$ ).  
 $\approx 1 \#A$  ( $stuns \ hes \ Eto \ BtQ$ ).



$00u,$   $U -$   $T - 100nA$ ,  $Ohon \ Bt \ \{\%00$   
 $\}, \ ., \ d \ i \ c \ \gg$ ,  $std, \ eS \ nlh \ \bar{z} \ B$ ,

---

$a \ . \ e \ \mathbf{l} = \mathbf{l}e = 1000l - 10mu$  ( $@lecho$   
 $ho \ \#B$ ).  $Ve = etc - 10m$   
 $(stL, \ hbass \ \{\gg \ Etc$ ).

$$[27] \quad a) \quad -5.0\% = -5.8V, \quad |z| = |T| = 50A$$

$$Z_c = I_c T = 40A.$$



**S**  $(\tau = 0.001 \text{ s}; G = 0.1 \text{ S}; I = 1 \text{ A})$   
 $(1) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(2) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(3) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(4) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(5) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(6) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(7) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(8) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(9) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$   
 $(10) i_o = 0.5 \text{ A}, U_e = -1.07 \text{ V}$

$i_v = 5 \text{ A}, U_e = -5 \text{ V}$   
 $e = 2 \text{ V}, i_c = 10 \text{ A}, U_e = 2.413 \text{ V}$   
 $i = 5.3 \text{ A}, U_e = 5.3 \text{ V}$   
 $(1) U_e = 2.628 \text{ V}, i = 1 \text{ A}$   
 $(2) U_e = 1.8 \text{ V}, i = 1 \text{ A}$   
 $(3) U_e = 1.8 \text{ V}, i = 1 \text{ A}$   
 $(4) U_e = 1.8 \text{ V}, i = 1 \text{ A}$   
 $(5) U_e = 1.8 \text{ V}, i = 1 \text{ A}$   
 $(6) U_e = 1.8 \text{ V}, i = 1 \text{ A}$   
 $(7) U_e = 1.8 \text{ V}, i = 1 \text{ A}$   
 $(8) U_e = 1.8 \text{ V}, i = 1 \text{ A}$   
 $(9) U_e = 1.8 \text{ V}, i = 1 \text{ A}$   
 $(10) U_e = 1.8 \text{ V}, i = 1 \text{ A}$

$$\frac{1210}{a} \left( I_{at\ e a} = 14 = 750 \text{ j} \cdot r_{i o w} \frac{260}{q} = 4 \cdot J \right)$$

$$e, - 100 \times 0.46.04 M k.$$

$$D r = -1 - 0.00 \zeta \left[ \frac{z T 0. 6.04}{g m, i} \cdot r_{g} \right]$$

$$= -1 - (070 + 0.84) = -2.567 \text{ V.}$$

$$(0) \alpha, \cdot e n - 5/4 = 1.26 \text{ A} (= 50 \times 0 / a w);$$

$$\pm - 0 o h \cdot 702 B \}$$

$$O r = -1 V - [(123 + 00 - 8) r V + (04 + 1.60 - 198)] a v$$

$$= -4 - (0765 + 007) = -2,672 \text{ /.}$$

$$H \cdot I \cdot @ u e - r_5 \% Y e e / 6' (+ z,) = h e W T \gg V.$$

$$(5) = (0 u s) [(e ? / h r s) / (t + 5 t 9)] \cdot 1.0875 \text{ a u h}$$

$$I C . o a r ) \{ (+ / 6) / (r s 576) \} - 0.95 a.$$

$$\rangle A T -- 5 \cdot c / l e -- 2 (29) = + 50 \% V$$

$$V e = 7/7 + 50 - 767 N.$$

$$F r O, 7 w k = (a 4 A) (2 / l e) 70 N e e = + 1 - 60 - - H 2 \Lambda;$$

$$2 - 50 - 25 + 25 V = 0 N o p - 2 (5) e - 50 N$$

$$4 V \% b y -- 2.60 -- 2 m l; V e = 7 l - = 6 \% V.$$

$$N e e b) = \& + 8 - 2 (40 - 9) = \% \% V; \forall e = 72 V.$$



E1 @ 306-2n'2<sup>B</sup> ( p#\$, ) = 1We 4so5v.  
 9 1 (9/09)x[ +BsL0+5) = T-r A.  
 re(e O{+8ta[(Is)]- JJ -  
 (°) 20 **O**k- 500A 2/lo = 4Ve--+188-68--442%1,  
 AT- 16- 9C, Ave = (2»v) - -00; W (to  
 = -H-100=- 1H2 a1, V %&0-2= 53& Z,  
 (U) T=55-2530·¢. " }a\_news p» PC 6.1.d  
 ad **500A)** t'Use ta00ane ve9, 302=%0  
 a.v, n lase **it** 680 -60=620al. Ue e&  
 aisle.B. err, do, ask t\_a to&t 60aNS,  
 iog ' ifls **∅** Tc, \$ 1 = low5so  
 =5% .

[T] @ s.% \$=1H, Tc=(re=ox?

=1100 »A; Vc- l; -lc-5-21770=1.5%V.

@ 9%at-g, et 6 80rWve, fps15bV ta sV.

mi Tc-k(Vee/V), ne 'ho

1.720 = k(+ .5%/100), I = (+ 5100)

I/.70 - (+5/0)/(1+15%) => Ic=1.78 A.

@ ) 1% = 73 = .5A, = pe e=2-05.

0.28%W, V=5-10x0282.13 V.

[T] @%. 5=2, e= .9, = 3

=Z . 2/0. 043 [o.

7, -1 — 2a5?e ( /w) - 2.n% A.

() Va- IV, Te-2 »P, V 2. \90 V, T=(5-2.50)/1-@.05aA

2.05/2 = +2950/09)/(1+1.0/%) => V= 77/.

@) -G 2)/o-0.A, Ig=/5-07/0-0.3 »A


= .3/0.13 z2.



$E = I_a \gg \dots = e \dots = 5$   
 $p \gg (5/0.0r = it5. (sh) o? = e \dots$   
 $55 \text{ kA. } \textcircled{O} V = AM \dots = 735 = 80V$   
 $\ll R' = 35/0 = 03s \gg A; T = 5, \{ Os, pc \}$   
 $05/0.65 = 17.$

$\square$  /a)  $CO = 1c - (07-02) / = 1.00 a\#$   
 $\dots - 100s/8 - (5.$   
 (b)  $V \dots = V_0 \% \sqrt{I} \dots = 3.$   
 $We = 6co - 12. \phi - 4. \text{ £am. } Tc - 1w, \# \ll - rzak$   
 $9 = 4 - a. \dots s - \dots \% \cdot ev.$

1

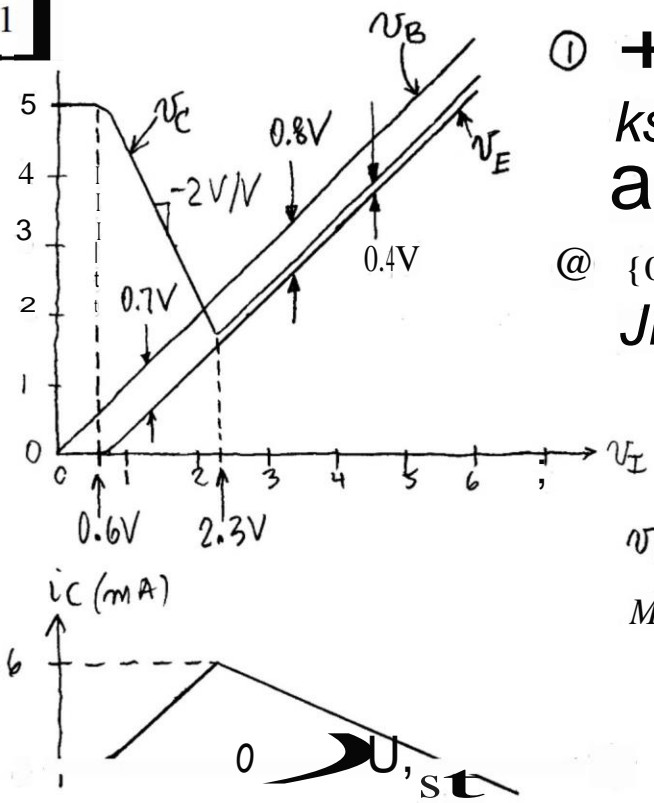

①  $+@ < V_{CO} \phi y$   
 $ks 8122i ct \{ \sim,$   
 $a = 1, > V, dc = 0.$

@  $\{ 0i5054 \sim aloe 0.eV$   
 $Jr \gg \gg tAT a.$   
 $7ala0Ms, t ho$   
 $vi rA, done$

$v = s - Ve_{0.} = 0 - 0.7V.$   
 Megown,  $C - V - cdc$   
 $zV, - Cc - \%, - e'$   
 $v - E_{Te} \text{ or}$


$\phi = 7\% \cdot \{ tees - \$; e. (ate, tkw \angle te . S.$   
 $Ao as l \cdot [ - Rahe > - 2V // 1. p.$   
 @  $k 5T rah \gg \gg ke \cos Ra \angle. s = (g19, n$

$e = \%v. t 1do Wt, (ra e + 0. = 18V) de =$   
 $t. + 0.72.3V - - ke \angle = (-1 \& / 2 - 1. \% + A$   
 @  $A \ll e \gg on \ll wig, tkJ ala \& \gg, Ok$   
 $a - r - 0. \& V, - e + 0. \cdot, - 0V, and \bar{f}$

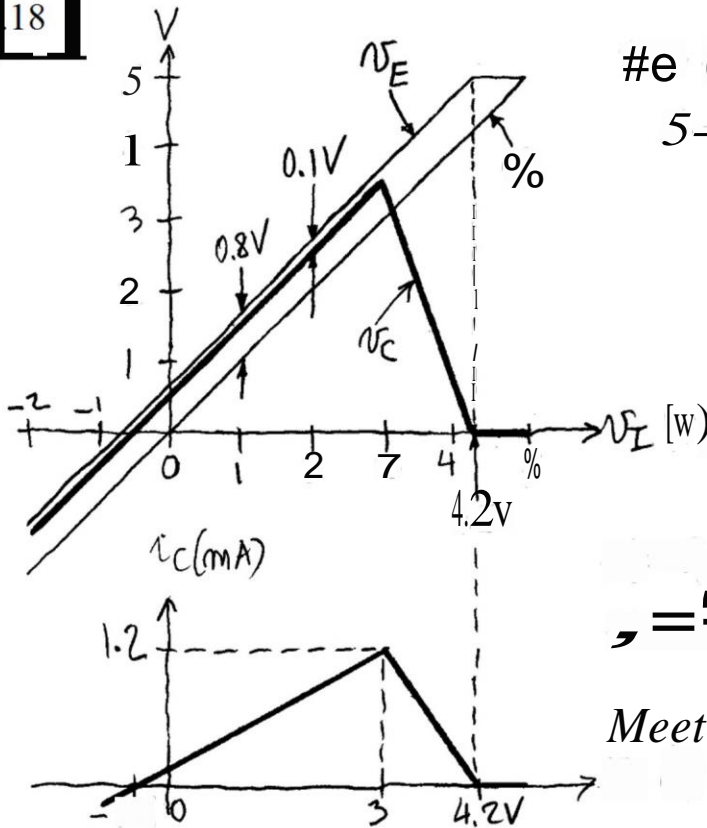$(6 - e) / 2 = [5 - (-0.2)] / 2 = (5.7 - \gg) / . Conk,$   
 $newd9waneo Wt. AF,,$   
 @)  $A \rightarrow rAko 5V ic det lo eus. Fd \pm > 5.7$   
 $\ll C 8com m3sky, \%e5 - Cuna. aio \{ oa. A$   
 $lass. , on \gg k ic 0VO owt 4 U Modsh !$







#e Oh, >  $V - V_{s(cc2)} = 5 - 0.8 = 4.2V$ ,  $B\beta = C_0$

$I_c = 0$ ,  $i_c = 0$ ,  
Loron, Oz 1 ear

4.2V  $\beta$  BJT

$m, \gg \gg$  otale, A,  
 $\beta$  & hue

$= +e / = (r + 0.8V)$

Meet 8n,  $U_r = C_{u} k c i c$

$\beta \cdot V_{R_a} S_e$

$= " " 2(-0, -08$

@ - 3 (42-G). (eanl, «o r 2» lonewed below (al,

We oicce»op adtl.els.  $A + W V$ , ad.  $C_{m} 0.8$   
cttl nsh  $4(v / (1y - (aAN. C_{C_{000}} i Ulin.$

0. - } e, tt 6A do » ta 05.  $W W K$   
 $\beta \cdot n 3(- (c + 08) - 0. ' , e \}$  kd l st

%0 BJ 1 % tale » tts 605 { - 2. '75 3}. 'Attwo

$m \sim C \cdot 4, \$32 (2-3) = -1.2 \gg A. 10 +$

cel.r

Vdinwo tli mo?e al mole ts <lnaos,

$9 re = 0e - 0.1 = + 0.8 - 0.1 = r + 0.7V, i_c > 0 / e =$   
(@ + 077) / (31).  $0 \gg e 1; 2 \gg$  lsonolt » -0.7V, ~cleav»

0, 01 Tr mes - (t.  $U$  i. kl, ks rs - c

$'yncia)'s < -0.a.$

[.19 J, «, ]

I  $g < 0 \cdot V > \text{BSTCo} = \dot{c} z v s 0, c - 6V,$

•  $S > 0.7 / \Rightarrow \text{BTO}, v w i l c l 0, \text{FA} :$

$i e - 's 8, \% - \frac{f f}{(r t - \frac{10 j 1}{j})} \geq -D 7 i c - p i e = \frac{0}{10} = 0.7.$

$e = \pm p o - - s + 2 [ = g 2 ).$

(@) **a** We noa.dawn,  $e s - V e \sim (e s) - 0. - 0.1 \text{ } 0,6 l, \text{BJT}$   
nuadwo eos. **th** » **post**,


$e o e - 4448 \% \ll k, V e 9 - 07 + 11 e t e e )$

$07 + P a s ) = 0.7 + 2.8 - 3.5 V ; = X ; \} = 2 A.$

+ )  $r e , > 35, \text{BJT} = \text{Sat} : i c = c o s ) - 2.8 s h,$

$a, - " s - 07, i, - e - i c = - 0.7 2.8 - ( T > - 35 \% \#.$

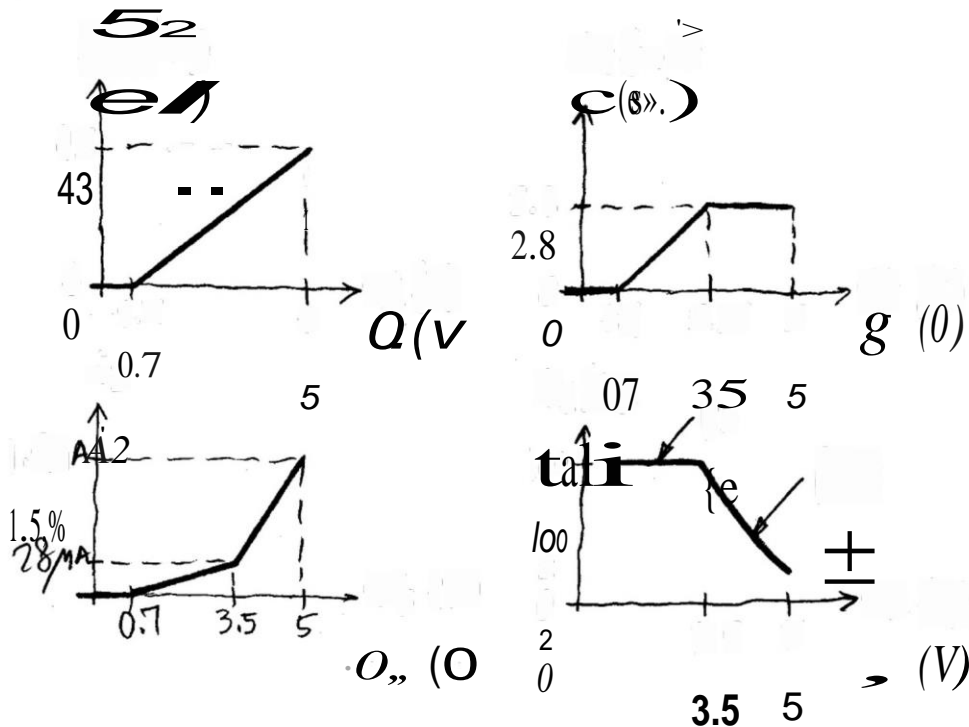$t c - \frac{2. @}{f. a, t u v s}, \frac{2, m. r}{j - z e l 1 b 8} > U 8$






2 @

WV1:  $V_{cz} > (c1 + 1ce @ E es = 10r2 + 2 + 2((rs)8;$   
 $kt \quad v - fP + Ve / (& es = 300 \gamma + 01 + 2(+ ;$   
 $== 3+) 1\%, z = o2 + 2p2) B =$   
 $z - 0? > ( = 10$

k

(b)  $L: s = 1tc + 02 + 2Te^{VE}$  ad  $1c + 02 + 2IE402 + 1c$   
 $= le : 5 - 02) / 3 = 1. \% uk \quad 216 - . 2V : V = 32 + 0 =$   
 $3. V ; P = 1.6 / 3 - 1.2, Ke (\$ - 3.9) / . 0 - 0.$

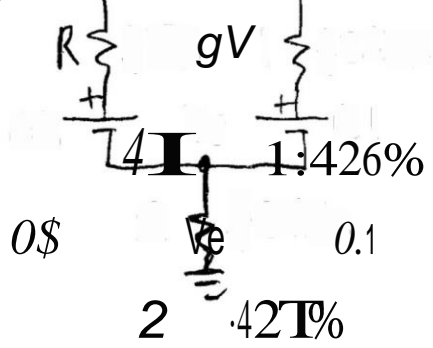
(9)  $d = 10 / s = 2\% = Tc = 2\% P te = 34 te.$




$5 - 1 \times 261 + 0. + 5 \setminus 1e \quad 1 a - 61.25 A,$   
 $Vg - 540.062125 + 0. \& = 3.4075 V.$   
 $R = (-3. \# 019) / 04175 \rightarrow 14. \bullet$



16 [a, &].

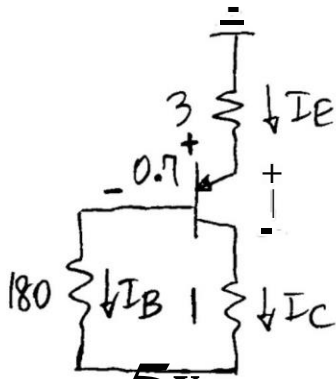

( ) S4

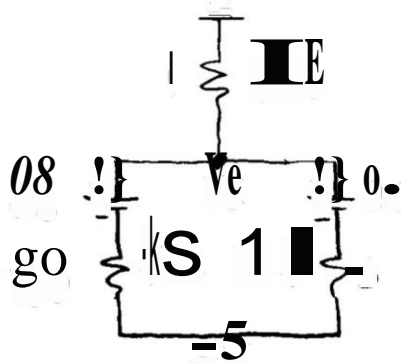

$$I_E = I_B + I_C = 0.1\text{mA} + 1\text{mA} = 1.1\text{mA}$$

$$V_E = I_E R_E = 1.1\text{mA} \times 3\text{k}\Omega = 3.3\text{V}$$

$$V_B = 0.7\text{V} + V_E = 0.7\text{V} + 3.3\text{V} = 4.0\text{V}$$

$$I_B = \frac{V_B - 0}{180\text{k}\Omega} = \frac{4.0\text{V}}{180\text{k}\Omega} = 22.2\mu\text{A}$$

Total current into base is 22.2 μA

$$I_B = \frac{V_B - 0}{180\text{k}\Omega} = \frac{4.0\text{V}}{180\text{k}\Omega} = 22.2\mu\text{A}$$

Re aueo (du BT% slut.

$$V_E = -1.237\text{V}, I_E = 1.237\text{mA}$$

$$I_C = 1.221\text{mA}, I_S = 1\text{mA}$$

$$I_C = 1.221\text{mA}, I_S = 1\text{mA}$$

$$I_C = 1.221\text{mA}, I_S = 1\text{mA}$$



$[ ] @ ) u : \% = v \% \% ) + @ , 9 \% + 8 \% ( 5 \% + 1 . ) .$

$1FA, 5=0+?0/e+3(1+/5)Lg+1%=7. @i t,$


$7c150x.0 > 1,6 U, Fe=1,37 t; kVI:$

$Ve0;7+200.000 -05a1.3% =0.3&1 - @ 13G.$

$Vd \% ) = -V_{cc}(\cos) -02 V_{0,2} = 0.88i - 00.916 \Rightarrow$

$0 \pm 0R, \pm 0.5Q.$

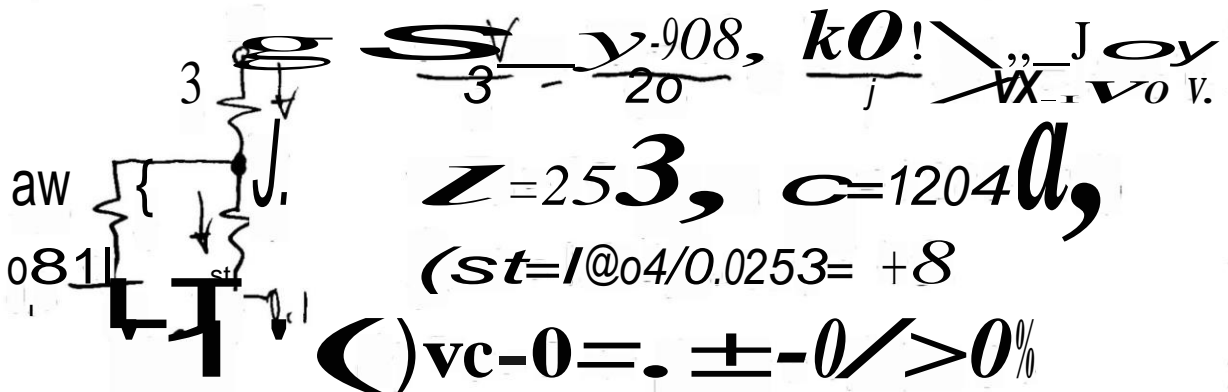$\bigcirc - 00.5 = I JT - < \% \pm > V - 0.1, Ve = 08V\%.$



2.23 (a) Assume FA, and check. By inspection,  $I_{R2} = I_B + I_C = (\beta_F + 1)I_B = 151I_B$ . KVL:


$$9 = 20(151I_B) + 100I_B + 0.7 \Rightarrow I_B = 2.66 \mu A, I_C = 150I_B = 0.399 \text{ mA}$$

$$I_E = 151I_B = 0.402 \text{ mA. By KVL again,}$$

$$V_{CE} = V_C = V_S - R_2 I_E - R_3 I_C = 9 - 20 \times 0.402 - 1 \times 0.399 = 0.567 \text{ V}$$

$$> 0.2 \text{ V} \Rightarrow \text{FA!}$$

(b) Assume saturation, and check. KCL:

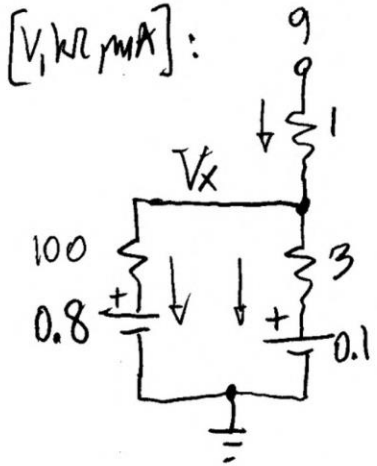

$$\frac{9 - V_x}{1} = \frac{V_x - 0.1}{3} + \frac{V_x - 0.8}{100} \Rightarrow V_x = 6.73 \text{ V}$$

$$I_B = \frac{6.73 - 0.8}{100} = 59.3 \mu A$$


$$I_C = \frac{6.73 - 0.1}{3} = 2.221 \text{ mA}$$

$$I_E = I_C + I_B = 2.28 \text{ mA}$$

$$\beta_{\text{sat}} = I_C / I_B = 2.221 / 0.0593 = 37 < 150 \Rightarrow \text{Sat!}$$

2.24

(a) [V, mA, kR]. Assume FA. kVL:

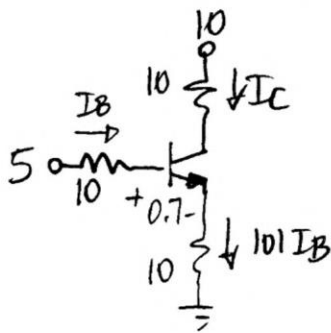

$$5 = 10I_B + 0.7 + 10(101I_B) \Rightarrow I_B = 4.2 \mu\text{A}$$



$$I_C = 0.422 \text{ mA}; I_E = 0.426 \text{ mA}$$

$$V_B = 5 - 10I_B = 4.958 \text{ V}; V_E = 4.26 \text{ V}$$

$$V_C = 10 - 10 \times 0.422 = 5.78 \text{ V}$$

$$V_{CE} = 5.78 - 4.26 = 1.52 \text{ V} > 0.2 \text{ V} \Rightarrow \text{FA!}$$

(b)

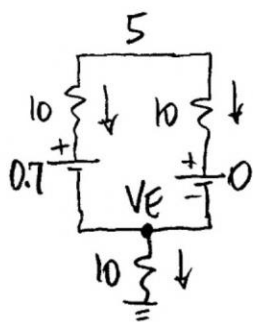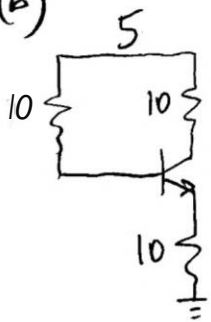

Now  $\beta T \sim \text{scale A,}$

CL


$$\frac{5(e^{72})}{10}, 5 - E \cdot \frac{V_E}{10}$$

$$2 > V_e = 31 \text{ V.}$$

$T = 0.12 \mu\text{A}; 11 \mu - 0.12 \mu \rightarrow I = 0.4 \text{ A. } X + @_j \cdot -!L$

(c)

& voe qcoe mole. kVL:

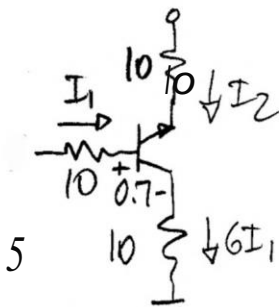



$$5 = 10I_1 + 0.7 + 6I_1 = 16I_1 + 0.7 \Rightarrow I_1 = 0.275 \text{ mA}$$

$$I_2 = 5I_1 = 1.375 \text{ mA}, I_3 = 6I_1 = 1.65 \text{ mA}$$

$$V_e = 5 - 10I_1 = 2.25 \text{ V}; V_c = 10 - 10I_2 = 2.75 \text{ V}$$

$$V_{ce} = 2.75 - 2.25 = 0.5 \text{ V} > 0.2 \text{ V} \Rightarrow \text{FA!}$$

(d)

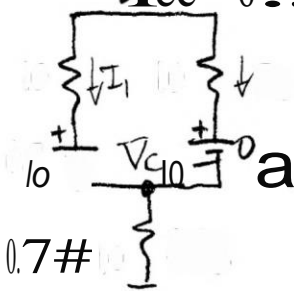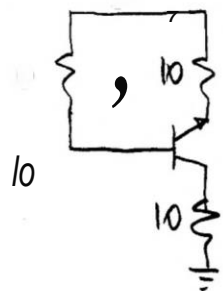

$$5 - 6.3 - 0.7 > 0.2 \text{ V} \Rightarrow \text{FA!}$$

$\beta T \gg p2 \& e - ode$

lo << las. **so!**

oi.cad bo >> OX >> kcllant ( ),


$$e = .v, I_1 = 0.12 \text{ R}$$

$$72 - 0.1\% \text{ ah, } [st =$$


$$0.1 / 0.4z = 1.G \cdot$$




[S] [A, ~].

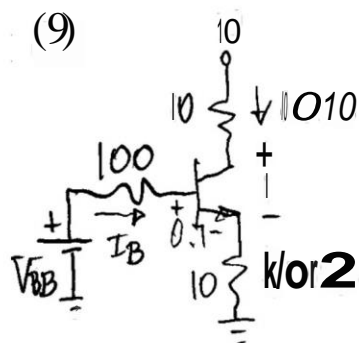

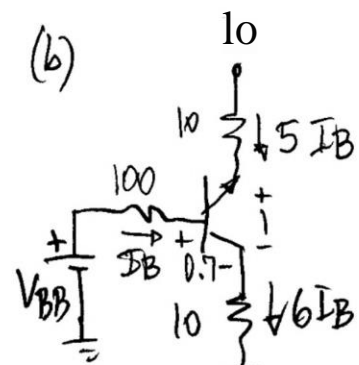
(9)  $V_u: 10 - 10(I_C) + 0.7$   
 $= 1\% = 44 \mu A$   
 $V_{CE} = 10 - 10(I_C) = 1.522 V, V_e = V_{e+0V}$   
 $- 5.22 \approx V_{e/e+0.2s} = 5.7 V$



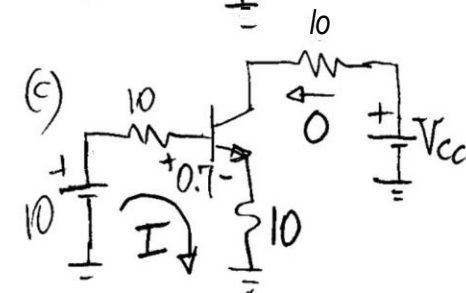(b)  $V_t: 0 - 10(5I_B) + 0.7$   
 $I_e = 81.8 \mu A$   
 $V = 0.7 - 10(I_e) = 5.61 V$   
 $V_e = 5.61 + 1000 \cdot 0.08 = 13.8 V$




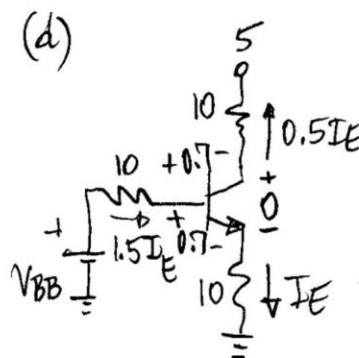(c)  $V_{CE} = 10 - 10(I_C) + 0.7$   
 $I_C = 0.05 A$   
 $V_{CE} = 4.5 V, V_{CE} > 5.3 V$   
 $I_C = 0, V_{CE} = 0.65 V, I_V$



(d)  $I_C = 15 I_B = I_C - 0.5 I_E$  (ode/clots)  
 $\Rightarrow I_C = (0.5 I_E) / (15 - 1) = 1 \mu A$  et.  
 $V_{CE} = 10 - 10(I_C) = 0.5 + 10(0.5 I_E)$   
 $> I_E = 1 \mu A \Rightarrow V_{CE} = 10(1.5) + 0.7 + 10(0) = 5 V$

22 « [ @ l, a ] .

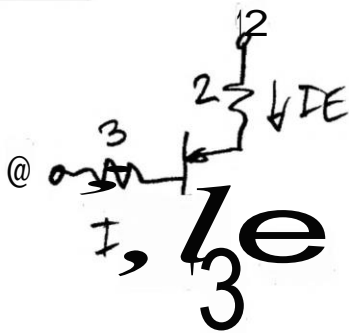

Yoe th:  $V_L$ ;

$$12 - 2 \times 5 I_C + 0.7 + 3 I_E + \dots$$


$$\beta = 7 \text{ MP}, \beta = 2.6 I_A,$$

$$- 2.42 \text{ aA}, V = 602 \text{ V},$$

$$V_{E67529} \bar{I} \cdot \phi V$$

VecauV 0.1 VcA!

)

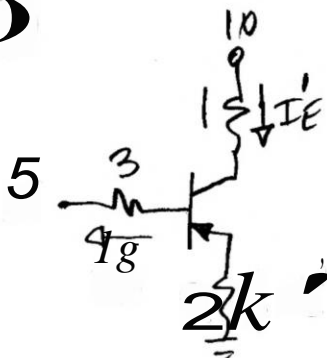

Assume RA: kVL

$$10 I_C + 0.7 + I_B + \dots$$

$$= 2 \rightarrow 0.5375 \text{ a\%}$$

$$I_C = 2 \times 0.5375 = 2.15 \text{ A}$$

$$I_B = 2.15 / 7 = 0.307 \text{ A}$$

$$V_C = 10 - 10 \times 0.5375 = 4.625 \text{ V}$$

$$V_E = 2 \times 0.5375 = 1.075 \text{ V}$$

@)



Puna Sb;

ucL;

$$V_C = 6 - 3 I_C$$

$$V_E = 1 + I_E$$

$$V_C = 1.736 \text{ V}$$


$$I_C = 1.736 \text{ mA}$$

$$V_B = 1.036 \text{ V}$$


$$I_B = 1.036 / 3 = 0.345 \text{ mA}; \beta_{\text{sat}} = 1.736 / 0.345 \approx 5 < \beta_F$$

$\Rightarrow$  Sat!


2 out, a

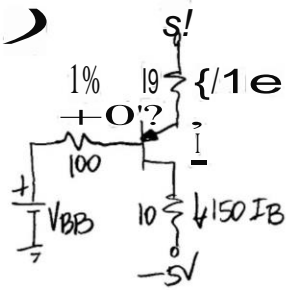

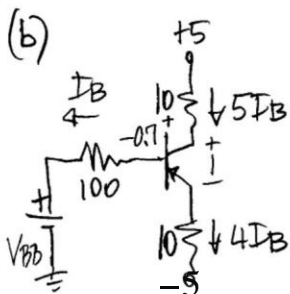
$I_{B1} = \frac{5 - (-5)}{100 + 10} = 0.1 \text{ mA}$   
 $I_{C1} = \beta I_{B1} = 100 \cdot 0.1 = 10 \text{ mA}$   
 $V_{CE1} = 5 - I_{C1} \cdot 10 = 5 - 10 \cdot 10 = -95 \text{ V}$



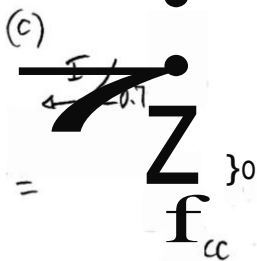$I_{B2} = \frac{5 - (-5)}{100 + 10} = 0.1 \text{ mA}$   
 $I_{C2} = \beta I_{B2} = 100 \cdot 0.1 = 10 \text{ mA}$   
 $V_{CE2} = 5 - I_{C2} \cdot 10 = 5 - 10 \cdot 10 = -95 \text{ V}$



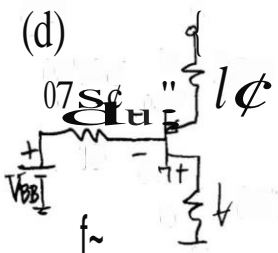$I_{B3} = \frac{5 - (-5)}{100 + 10} = 0.1 \text{ mA}$   
 $I_{C3} = \beta I_{B3} = 100 \cdot 0.1 = 10 \text{ mA}$   
 $V_{CE3} = 5 - I_{C3} \cdot 10 = 5 - 10 \cdot 10 = -95 \text{ V}$



$I_{B4} = \frac{5 - (-5)}{100 + 10} = 0.1 \text{ mA}$   
 $I_{C4} = \beta I_{B4} = 100 \cdot 0.1 = 10 \text{ mA}$   
 $V_{CE4} = 5 - I_{C4} \cdot 10 = 5 - 10 \cdot 10 = -95 \text{ V}$

$V_{CE} = 5 - I_{C} \cdot 10 = 5 - 10 \cdot 10 = -95 \text{ V}$



$I_{B5} = \frac{5 - (-5)}{100 + 10} = 0.1 \text{ mA}$   
 $I_{C5} = \beta I_{B5} = 100 \cdot 0.1 = 10 \text{ mA}$   
 $V_{CE5} = 5 - I_{C5} \cdot 10 = 5 - 10 \cdot 10 = -95 \text{ V}$


$V_{CE} = 5 - I_{C} \cdot 10 = 5 - 10 \cdot 10 = -95 \text{ V}$

$V_{CE} = 5 - I_{C} \cdot 10 = 5 - 10 \cdot 10 = -95 \text{ V}$





[228] [v, aka]. os»L90-A.1ez,,0s=0.s1»A.

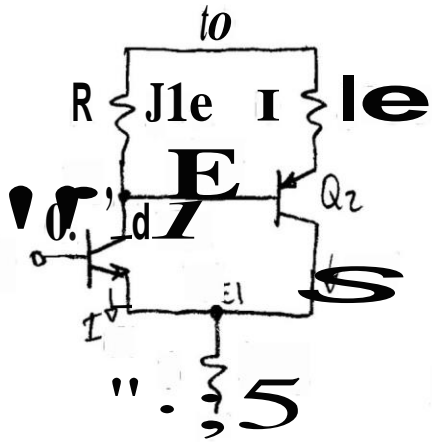


vte  $V_{e-10-10 \times 0.51} \rightarrow$ ,  $V_{I}$ :  
 $V = 4. - 0.7A. 2V = V_{e}$ .  $\beta$ :  
 $T_e = T_a - 1\% = -0.105 - 0.1\% A$ .  
 $w? \gg e? + . \alpha$ :  
 $11\% - m\% - 95 - \# \} A$ .

$0.11mA$ ,  $R = \frac{10}{700} = 10 \mu A$ .  $V_{ce} = 4, 1 - (4 - 0, \beta I_c) > 0.2 V$   
 $= 0 - A. V_{ce} = -(-0.7) > 0. V > G = FA$ .  
 $\beta = 1 = I_c / I_b = (52) / 55 = 10' 7 A$ .

[229]

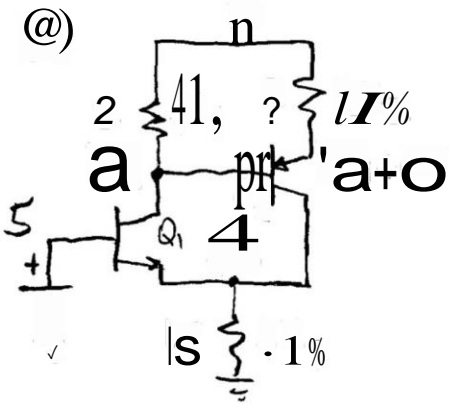[4k]. As  $\gg \ll eQ, O = FA, O \gg d$  cu-k.  $V_e, V_a, =$



5-07-43V. 170wig,, bane croon»ho,

7, -Te **a** : **I** la, «


$$\frac{I_z}{1.5} = \frac{2 - V_a}{23}, \frac{r - (Nao \cdot D)}{2}$$

$$V_a = 2.0V = I_{ee} 1, - R_{II} =$$

$$n a, m \dots \sim I = \frac{12 \cdot S}{4} = 0.7 =$$

1

$$1.5nA, e - 2u - 43 \dots$$

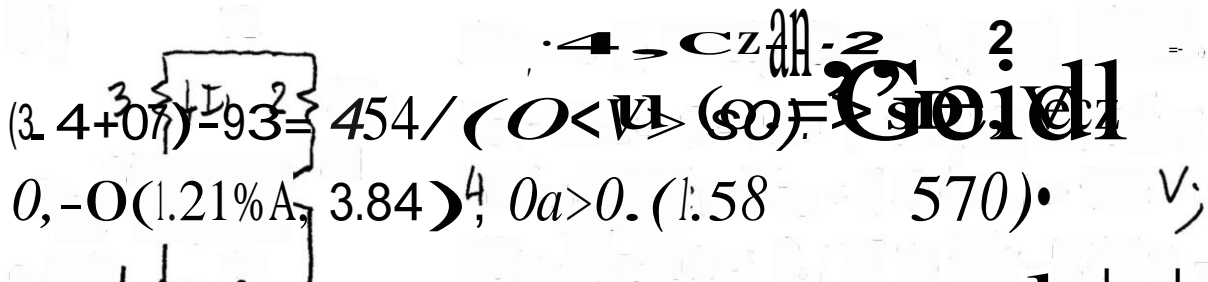

(%)

$$I_a''' \pm, \dots$$

karc @ **st** Q7A, al ck»ck.

$$V_{et-ca} = 8.07 - 7.3 / 7, 0.3 / 5 =$$

$$1 \gg -v \gg -1. + a = n$$

$$W_e = V_a + 7 = 8.1 V I (7 - 70) / 3 =$$

$$1.53mu, T_e = (2 - 8.) / 2 = 1.5\%h.$$


$$0 - 0(1.5A, 0.8V), FA. kcI$$

$$J_r = 1, - (1,) - 481 - (53 + 115) - 1.38\%A. F/en, £$$

$$2/1w = 15/18 = .1 = 0 = t, al 0 - (1.53\%4, 0.1V).$$



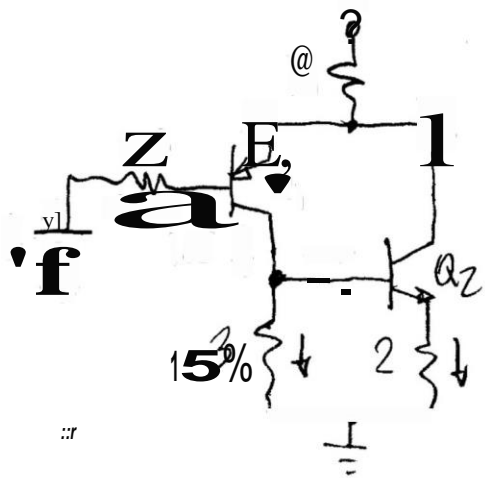[2.3] @) 1 - A ] : 0 : 1 -  $v_e - 1\% + re_2 l()$



$v_e \cdot 1g, \dots Na; 0 1, \dots -4.7\%$

$e \cdot \frac{4}{50} = 0 - 1.85\% A$

$I_v \frac{50}{2} = 18 / A$

$5le \dots \%$

$er5r = 5is - ta$

$geT_{cp} . 31ank$

$I - 70/9 \dots 6/0 = 0.0, \dots V_{ey} - 6 + 320, 0 - 4. / ;$

$V_e - V + 07 = 1.6, \dots R_r (12 - 7.6) / 33 \text{€} 1. \%$

$(wh: W_e - (2 - 138339) - 4.34 \text{€} 33V > 0 / = FA.$

$W \text{Z} (12 - 1.3433) - ((3 - 07) < 4 / 0. W A.$

$() kw ) \& z00. daa0a le mud, vek vS$


$olds.tog tko \gg bag, \dots ow - Vows,$

$V_e \quad 1 s s V, T_e, is'07) / = 1\% h', T, =$

$l.s+ \dots = 3.\% k; R, - (2 - 1.6) / 3.4 = 127 inl. 3k0.$



[231] {v,%4)}. koms 00-FA, nu Reh.

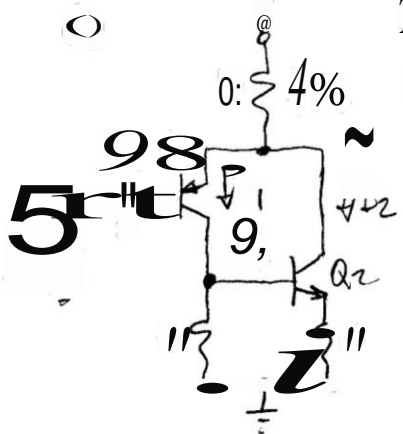

Tei} PaPl. Lsz, we hae, b8kl,

Ve-Ve -%+07e 5+0.7- 57/. n:

»=(-5/0=0.6mA. ct:

7+, =04=j, "  $\frac{V_e - V_a - 0.7}{10}$


%we-S1-7;-0.

Jc-063--035 0287MA.

lea-551-35-2.2V > 0 V Ft, Ve, =57-(5-0.)

0(0&A, .). 18, qe 0(095A, 2.20); 02°

0(0&A, .).

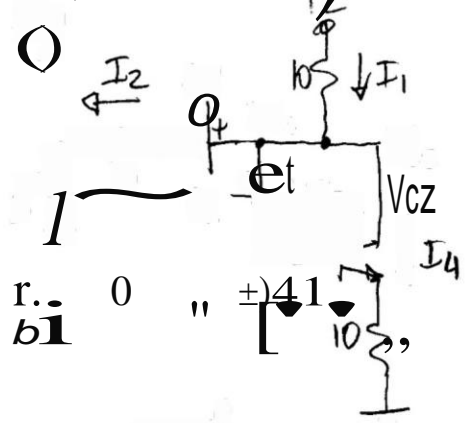

wti R, evkedfo aua,, Te

72e2 = w Snell, 5 nu

Pvt kl/, L- Ar:1 ::r-u

D,

ii/dis, Ve2=07+0>

08V > 0.1VOA.

IK=VVc. oL

$$\frac{1}{11} \times \frac{1}{J-z-r}, \frac{1}{L}, \frac{1}{+T:4} - r_z.v \text{ //, t.l..}$$

$$\frac{1}{10} - \left( \frac{0}{10} \right) 5, -09-0 \frac{1}{10} V-6.(v \frac{1}{10})$$

$$1 - .40\text{£}-g05-00 \mathbf{i}, , 1 v90$$

$$=052A. I_a=7=1 [r. W^g, pez)$$

$$hs. \mathbf{it} Te < 0.575/co53\%A \mathbf{pl} + < 5.3\%$$

$$0.1 \mathbf{O} > \ll k. Tu0w \gg, Q-0, (< 5.36A, 0IV), ad$$

$$00(0.53\%ah, 0.8v).$$



[3h, , , al. Use  $U$ , oh' horpsh.dy.

$$V_{cc} = Rca + V_{az}(eos) + ks [g \cong (@u+@g) cz + V\sim c(o) \Rightarrow$$

$$5 = 22I\phi^2 + 02 \quad D_z^2 = \phi.77 \text{ m\#}$$

$$I_e = I_{in} - (V; V_{ea} = 0.7 - 0.7 = 0.07V = V_{e.}$$

$$e - 47/0 - 7.7 \phi -$$

$$I_a = (5 - 0.0z) / 30 + 62.710? = 0.3\%52A. / \text{same } Q, A.$$

$$I_r = 0.3\%3/0 = 3.66A$$

$$V_{e;-} V_{\ll} - I_e, = 5 - 10 \times 3\%16?4.\%V$$

$$V_a - +6 - 0.7 - 3.9 \text{ V}$$

$$e | : I = 0.7 \text{ au} \pm$$

$$6\% = 0.9/0.37 = 105e$$

$$V_e \text{ } I_{o21} - 3.9 > 0.2 \gg Q = A.$$



33 |  $(\ln G, \{vt, rd\} \text{ scone } +A. vu@4, :$

$$I_y = \frac{5 - 0.57}{10 + 10} = 2.23 \ll$$


$$V = 5 - 1102.0306 > ZV; Wa - 405V$$

$$T\phi, = 100 \gg 0.3 - 0.223 \%A$$

$$I_a = 15 - 300.2 - 83 \setminus V$$

$$I_{cer} = 8.31 - 10.5 \gg 0 \Rightarrow Q = FA. \quad \text{let } ct:$$
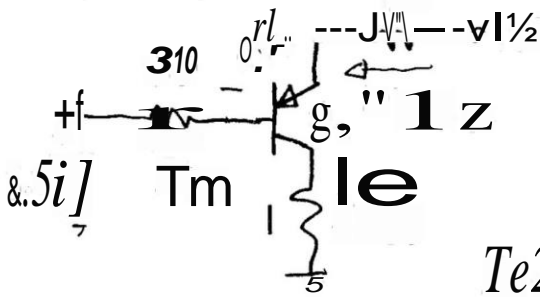
$$h \nearrow 0 = FA. \quad e \quad J, \dots \frac{15 - 8.3 - 0.12 \cdot 4}{(30 - 10)(1 - \dots)} \quad \text{A.}$$



$$V_e = -831 + 0.3 \cdot 46 = .5V$$



$$e_z = 9.g + 07 - .2V$$

$$Te2 \quad I_a = 100Be \cdot 9\% \neq$$

$$V_e = 1. \%z + 7. V_e e - 102 - l > z0.2 \Rightarrow = tA.$$

3

6) sy

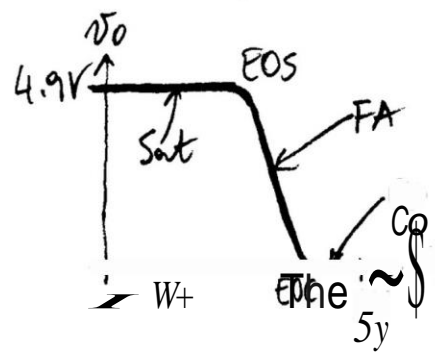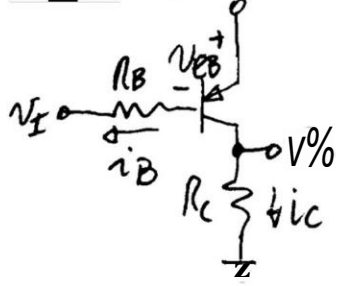

Te  $r > V - V_{esc} 0.05 - 0.6 = 4$ , tlo  
 87 200 c t [( . long, r  
 helar UV dcoth, E t oi. FA:  
 Di, - V - O - Sie

$$V_{ce} = V_{cc} - I_C R_C$$

$$= 5 - 0.0206 \times 77 = 1.08$$

$$r_{ce} = 5 - \{ -0.026\% (W'0:) \}$$

$$V_{ac} = V_d (s z) - 5 - 0.14, a /$$

ow>, soc p0. V c S - ; - 0oghu (on) = 3.628v.

( ) = s - # - 0026% ( " @ ) - 3.74%V

0% / 0# - + #% / 0 - aw e " # ; ) or

= - % - 00% \$ a - = 8 @ ; a | 0 - V - & 44 W.

2.35

$$(a) \text{ KVL: } v_I = R_B i_{R_B} + v_{BE} = R_B (i_B + \frac{v_{BE}}{R_{BE}}) + v_{BE} = R_B i_B + (1 + R_B/R_{BE}) v_{BE}.$$

$$(b) v_I = 10^4 \left( \frac{5 - v_0}{10^3} \right) / 100 + \left( 1 + \frac{10}{5} \right) 0.026 \ln \frac{5 - v_0}{10^3 \times 2 \times 10^{-15}}$$

$$v_I = \frac{5 - v_0}{10} + 0.078 \ln \frac{5 - v_0}{2 \times 10^{-12}}.$$

$$(c) v_I = \frac{5 - 2.5}{10} + 0.078 \ln \frac{5 - 2.5}{2 \times 10^{-12}} = 0.25 + 2.173 = 2.423 \text{ V}$$

(shifted to the right by about  $2v_{BE}$ 's).


$$(d) \frac{dv_I}{dv_I} = \frac{1}{10} \frac{dv_0}{dv_I} + 0.078 \frac{2 \times 10^{-12}}{5 - v_0} \left( -\frac{1}{2 \times 10^{-12}} \frac{dv_0}{dv_I} \right) \Rightarrow$$

$$1 = -\frac{a}{10} - 0.078 \frac{a}{5 - v_0} \Rightarrow a = -10 \frac{5 - v_0}{5.78 - v_0}.$$

@  $v_0 = 2.5 \text{ V}$ ,  $a = -7.62 \text{ V/V}$ . In the example,  $a = -9.06 \text{ V/V}$ .

Reduced gain stems from the presence of  $R_{BE}$ , which forms an input voltage divider with  $R_B$ .

»e

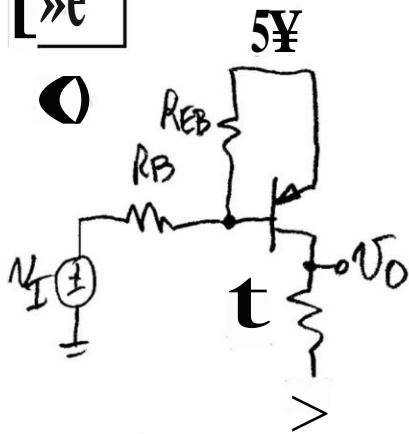

$$V_I = 5 - V_{EB} - R_B \left( i_B + \frac{V_{EB}}{R_{EB}} \right)$$

-5-6%-( $\$$ )es,  $\sqrt{S}$ ...  $\frac{\text{e}}{80}$  & 010?

Impose  $SS\% - (\%:$

+0or-; (. & es.

&) e-5-10#; -3roeo("@to") -

=5-}o- 0.07&. nlc"«ca). p./oo»dials wrb Or:


1= %2, -O&bee." #/

'> ±###- £  $\frac{d}{dt}$  %; #SS-

too, -75%,  $gm = \beta g_s = -10.7 \text{ V/V}$



[SS] @

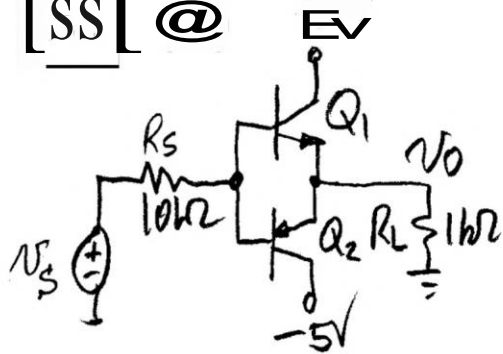

$V_C? i b i s, s o o w l - \{$   
 $t u c o n r o. [ , A j .$

$0 < 0, 0. \% = 0 = C o .$

$\rightarrow 0. V \Rightarrow Q, = E 0 c ,$

$0 < 0 < 5 - 0.2 = 4.8 V 0 = r .$


$0 = . V s 0 = \epsilon 0 \% , \gg . l$

$Z = 48 + 07 + R < L g$

$- 55 + 110 \cdot \# f$

$= 5.88 V . 4 + + + +$

$\Rightarrow V_0 = 5.55 / 0 + c h$

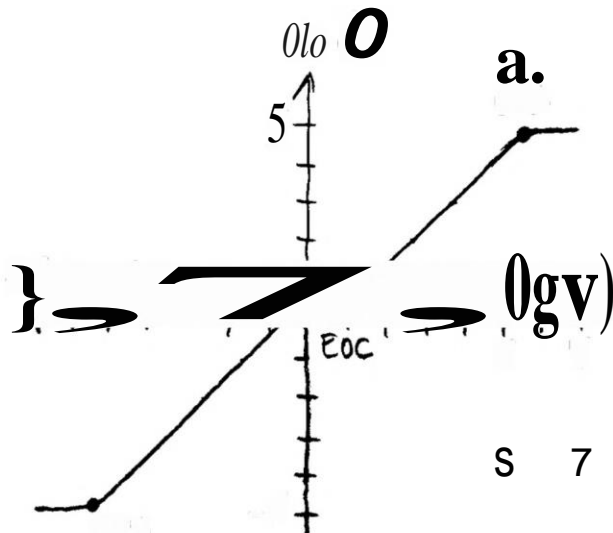

e05 -S

(e)  $\% - 2.5 V = U r - + 2.5 + 07 + 10^{-4} \% ) 7 \pm 345 /$

[ ] 6

A	8	@	G	'(
L	L	Co	Co	kH
L	H	Co	Sk	L
H	L	St	Go	L

(b)  $\beta_{F(min)} > \left( \frac{5 - 0.1}{1} \right) / \left( \frac{5 - 0.8}{10} \right) \approx 12$



2.40


@6

A	8	@	%	Y
L	U	Co	Co	HL
	H	C	Co	H
H	L-	Co	Go	H
H	11	%t	sad	L-

0- [74p.1/[ $\frac{0.8+0}{10}$ ]=7. %+


Z, [4<sub>0.1</sub>, +=44. # \.

2.41

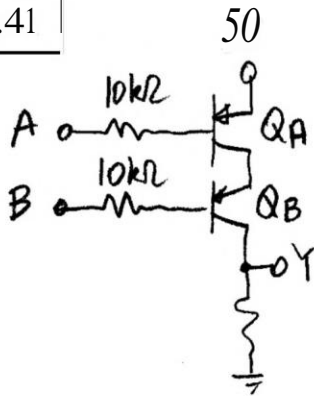

A	3	QR	--	Y
L	L	5I	\$k	H
L	J	O	Go	L-
A	L	Co	Co	L
H	H	Co	Co	L

2.42

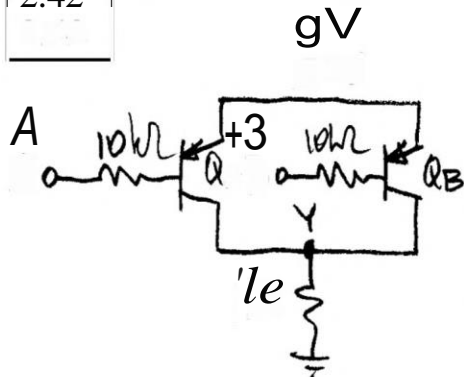

A	3	Q	S	Y
L	L	b	1	1/2
		Sal	O	H
k	L	Co	5	H
H	H	Co	Co	L




**1)**  $(5 - 1.5 - 0) / 0.33 = 103 \mu A$

$I_{(0 \gg)} = 10 \sqrt{50} = 0.20 \mu A$

$\&lt; (G - 0.8) / 0.20 = 20 n$

**(b)**

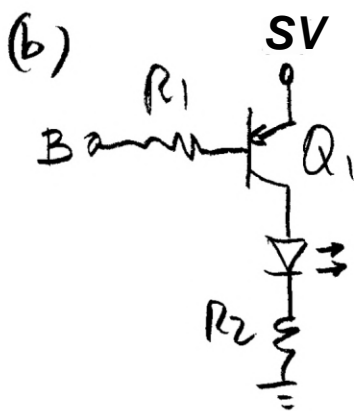

$3 = 1 - 0V > 0 - 5V = E_b \approx 9m$

$BH6 / 0 - C_0 \Rightarrow LE \sim \text{dank}$


prwrg, 7.e Sam. parameters

$no \sqrt{6S4}$

@ -10V, 11, 3309.



@) ssn:

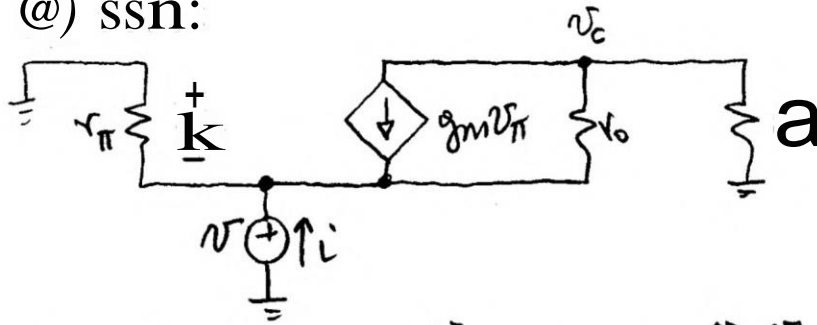

$$\text{KVL: } v_{\pi} = -v. \quad \text{KCL: } i + \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} + \frac{v_c - v}{r_o} = 0, \text{ or}$$

$$i - \frac{v}{r_{\pi}} - g_m v + \frac{v_c - v}{r_o} = 0. \quad \text{Supernode: } i = \frac{v}{r_{\pi}} + \frac{v_c}{R_C}, \text{ or}$$

$$v_c = R_C \left( i - \frac{v}{r_{\pi}} \right). \quad \text{Eliminating } v_c \text{ gives}$$

$$i \left( 1 + \frac{R_C}{r_o} \right) = v \left( \frac{1}{r_{\pi}} + g_m + \frac{1}{r_o} + \frac{R_C}{r_{\pi}} \frac{1}{r_o} \right) = v \left( \frac{1}{r_e} + \frac{1}{r_o} + \frac{R_C}{r_{\pi}} \frac{1}{r_o} \right)$$

$$R_e = \frac{v}{i} = r_e \frac{r_o + R_C}{r_o + r_e + (r_e/r_{\pi}) R_C}. \quad \text{Considering that } r_e \ll r_o$$

$$\text{and } \frac{r_e}{r_{\pi}} = \left( \frac{\beta_0}{\beta_0 + 1} \frac{1}{g_m} \right) / \left( \frac{\beta_0}{g_m} \right) = \frac{1}{\beta_0 + 1}, \text{ we get}$$

$$R_e \approx r_e \frac{r_o + R_C}{r_o + R_C / (\beta_0 + 1)} = r_e \frac{1 + R_C / r_o}{1 + R_C / [(\beta_0 + 1) r_o]}$$


$$(b) \quad r_e = \frac{100}{101} \times \frac{26}{1} \approx 26 \Omega, \quad r_o = \frac{100}{1} = 100 \text{ k}\Omega$$

$$R_e \approx 26 \frac{1 + 10/100}{1 + 10/[101 \times 100]} \approx 28 \Omega.$$

$$(c) \quad R_e \rightarrow r_e = 26 \Omega.$$

$$(d) \quad R_e \rightarrow r_e \frac{R_C / r_o}{R_C / [(\beta_0 + 1) r_o]} = r_e (\beta_0 + 1) = r_{\pi} = 2.6 \text{ k}\Omega.$$

# 4.1 S

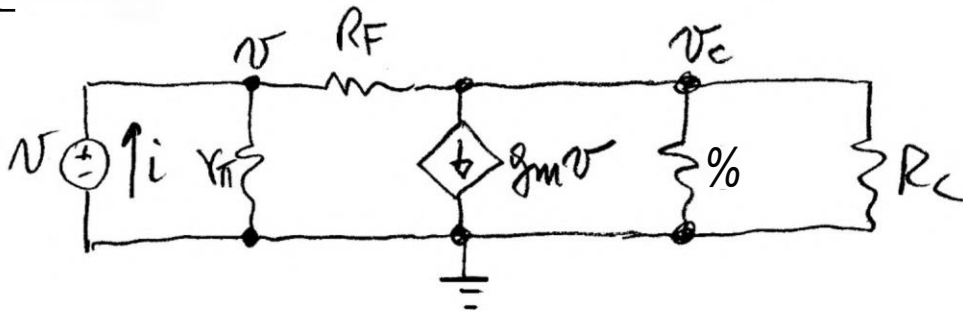

$$i = \frac{v}{r_{\pi}} + \frac{v - v_c}{R_F};$$

$$\frac{v - v_c}{R_F} = g_m v + \frac{v_c}{r_o \parallel R_C} \Rightarrow v \left( \frac{1}{R_F} - g_m \right) = \frac{v_c}{R_F \parallel R_C \parallel r_o} \Rightarrow$$

$$v_c = \frac{R_F \times (R_C \parallel r_o)}{R_F + (R_C \parallel r_o)} \frac{1 - g_m R_F}{R_F} v = \frac{R_C \parallel r_o}{R_F + (R_C \parallel r_o)} (1 - g_m R_F) v;$$

$$i = \frac{v}{r_{\pi}} + \frac{1}{R_F} \left[ 1 - \frac{R_C \parallel r_o}{R_F + (R_C \parallel r_o)} (1 - g_m R_F) \right] v$$

$$= v \left[ \frac{1}{r_{\pi}} + \frac{1}{R_F} \frac{R_F + (R_C \parallel r_o) - (R_C \parallel r_o) + g_m R_F (R_C \parallel r_o)}{R_F + (R_C \parallel r_o)} \right]$$

$$= v \left[ \frac{1}{r_{\pi}} + \frac{1 + g_m (R_C \parallel r_o)}{R_F + (R_C \parallel r_o)} \right]$$

$$R_i = \frac{v}{i} = \left( \frac{1}{r_{\pi}} + \frac{1 + g_m (R_C \parallel r_o)}{R_F + (R_C \parallel r_o)} \right)^{-1} = r_{\pi} \parallel \frac{R_F + (R_C \parallel r_o)}{1 + g_m (R_C \parallel r_o)}$$


(b)  $r_{\pi} = 100 (26/1) = 2.6 \text{ k}\Omega$ ,  $r_o = 100/1 = 100 \text{ k}\Omega$ ,  $g_m = 1/(26 \Omega)$

$$R_i = 2.6 \parallel \frac{10 + (1/100)}{1 + (1/100) 10^3/26} = 2.6 \parallel 0.281 = 254 \Omega.$$

(c)  $R_F \rightarrow 0$  and  $R_C \rightarrow \infty \Rightarrow$  BJT is diode-connected, and  $R_i = r_{\pi} \parallel \left[ \frac{r_o}{1 + g_m r_o} \right] \rightarrow r_{\pi} \parallel \frac{1}{g_m} = r_e \cong 26 \Omega.$

(d)  $R_F \rightarrow \infty \Rightarrow R_i \rightarrow r_{\pi} \parallel \infty = r_{\pi}.$

246] 955:

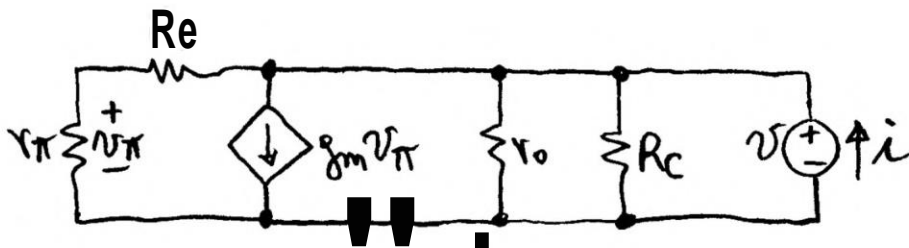

$$C: - \frac{1}{r_o + R_c} + \dots$$

$$\dots \{ \dots \} \dots \frac{3 \dots}{n} \dots W \dots$$

$$1 - \frac{v}{\dots} \dots \frac{K r + f r}{\dots} \dots ?$$

$$\dots \text{he}' R \dots 5, \dots \text{per } (5 \dots) \dots t,$$

$$i: 9 \# \dots S \dots / cl(e \dots \{i\})$$


2ca, - 00, @, - // 8 @ u4! [ ] 5 in.

@ & e 0, Ca) K, = // egte (T = ode).

@) W. 1 tkc lase t « e, On o « a }, > 0.

h 4 hrs., (G. > Kelk / @ c.

2.47 Apply test voltage v:

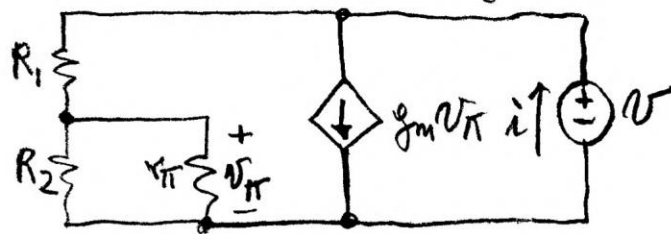

$$v_{\pi} = \frac{R_2 / r_{\pi}}{R_1 + (R_2 / r_{\pi})} v$$

$$i = gm v_{\pi} + \frac{v}{R_1 + (R_2 / r_{\pi})}$$


$$= \frac{gm (R_2 / r_{\pi}) + 1}{R_1 + (R_2 / r_{\pi})} v$$

$$R = \frac{v}{i} = \frac{R_1 + (R_2 / r_{\pi})}{1 + gm (R_2 / r_{\pi})} = \frac{[12 + (15/10)] 10^3}{1 + (15/10) 10^3 / 50} = \frac{18000}{121} = 149 \Omega$$



2.43] @ 6 dim,  $R = (+a \cdot Re - g \cdot 5 \cdot \circ)$

$K - @@ \ll [++ (39) ]$

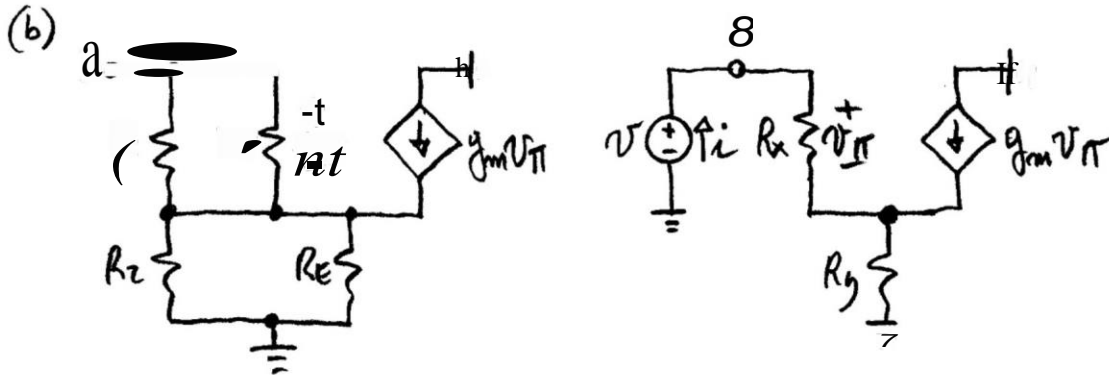

wd.  $t_d$  sold cbel  $\approx 9 \text{ tA cktks BAL}$ .  
 $T_{io}, T_s \gg$ , o **ašk** to  $v\%.t$  tkens@t,  
 WWila «e Jet 1 Rdo» ad  $R \gg$  @ **Z. ply**  
 a tot **ta, 0**» so., - gw, c1 &  $V_u$ ,  
 - " + ea «r - 'u'. d, or - &  $\phi$ . eta» ch,  
**ct&d**, el tlgythenado - **Oeo**

$K_v = \& + (+, 09)83$ .

(@)  $W = 1/(260)$ ,  $r = 2.6 \Omega$ . Fo  $ca(av)$  «w. **gt**

$\& - (0+) 1(7.\% + to t0) = 10. Gk (+ 2 \cdot)$ . **F**

$0ox(b) au gt (- 10\% = 20\%$ , , -  $10/105$ ;

$R = 2.00 + (+ - -')s - 6\%$  (**86**). Th» **i**

ma.A. - hew. ta. (6)! **ke wimp**  $\gg$   
 noise tkew vjpd **pa** « da » » sale~ht, !

$\frac{1}{2} \frac{d^2}{dt^2} + 0.2 \frac{d}{dt} + 1 = 6$ ,  $V_e(\frac{1}{2}) = 1 - V$ , «e-@-h=
   
 $1.601$ , wt  $9, -0 \text{ Ta}, 2 = (\frac{0}{\epsilon_0} = 20 \text{ A}$ .
   
 Thea«  $R, -101a - 0.2m4$ , ASsuwig  $V_e5(a) = 0.1$ ,
   
 me  $la$ .  $V_e - (-0.7) 53 / 0(-5.3) 0.2 - (8.5 @$ 
  
 $(we @u) al, \dot{=} 53 / (0.2 + 0.02) = 24 \text{ kn}$ .

(2)  $\& - |lf - 10.3$ ,  $Veg - 9 \gg 24 / 18 + 24$  )  $5. \text{NV}$ 
  
 $7, \frac{1e \text{ e } S - V_e \text{ o } W}{(8/g + \epsilon)}$

$Tc(\omega \nu \gg 0) y - \frac{-5. \& - 0.1}{103 / 100 + 1.5} = 1.7 \text{ A}$

$C\% a) - \frac{-5.1 (on 5) - 0.1}{(0.5 \sim @ 5 [s + 15(00 \frac{1}{5})]} \approx 2.3\% \text{ A}$

$CO) - \frac{@ - 5. (1. \text{gs}) - 0.1}{(9810s) / 5 + 15 [cs]} \approx 1.7 \text{ h}$

$(t 0.3 \checkmark - \pm 5\% \text{ eiadds a. } Tc)$ .

S


@)  $T_g = 2 \gg 1020 \text{MA} = IR,$

$R = 0.7 / 0.02 = 35 \text{k}\Omega$  (re 3%)

$g = \frac{20.4}{0.02} = 375 \text{Z}$  (e33k)

$\ll a = \frac{5.2}{2+0.0} = 11 \text{ la}$  (e Is#)

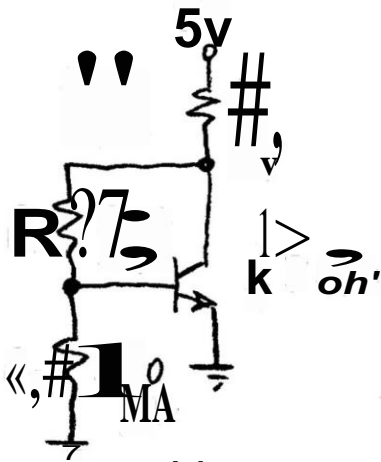$\} \cdot \text{c} \cdot \text{E} \cdot @ (S, \text{be});$



$V_e = 0.7 + 33(\% + 0.7/3\%) = 1.34 \text{ V} + (30)2\text{p}.$

$I = \dots = (e92) \cdot 51 \text{Z} = \dots = 22 - 231\% = 242 - 273 \text{ 7/54, p} \cdot \text{Fe},$

$I_C = \dots = 20 \text{ AL } I_C 1.6\%$

fr

A


1.1 «A, 2.(7 au 4. Net **Jal!** Mo2cu e=v:

1 + 1c/» = 2.41, 1V, 110V, al reefs  
iNolak rel 4 N.





[s] (e 1, -3/50 = 704, , -9, = 07/0 =

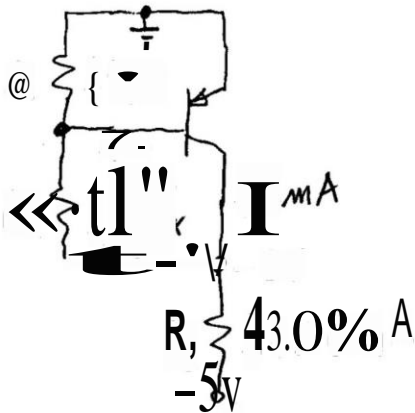

$mS(v|8)$ ,  $I_R - I_{R1} N7$   
 $3Pu, (-f07 - (3)\sqrt{0.0\%}$   
 $3zk (1a)$ . — Te  
 "112, ? + 0.0 G  $\sqrt{3}$ , obt#1A, Re~  
 $fa - (0/0 - 0\#8n(we1a)$ .

@ a. - 0 - 8(% + 4,) - " - (s + \$) =

$V_e = 0 - V_e - 0.211 + 3Is$ . @ = R - IR, or

$6 - I_e \cdot (e \cdot Q) - \% - @275i - \bar{s} - jg1^p$

$1c = 5\bar{4} - ova - 3:7 + -\#f1 = Te_z / (n;)$

$6 - ) = i\bar{0}/5 \quad 2 \cdot auk) \quad Lc_{f(w,} - \frac{27}{170} - 27\%$

mh} % or  $t \sim i - 2.3$  **Gorda'**

ec(as) - z.an + n(@4/19) - **.4V**,

le(>>) **2.8W** Vec(s>>) - **2.2 V**.



---


$$[a] @ r = re^{-(3-05)l} = 1.0 \gg$$

$$(9) V_e - T \exp(0he/t) - 10 \exp(0) = 1.080 \% A$$

$$@ T_e - I_a @ p(25/26) = 1\% 1 K$$

$$(a) V_e = 0_0 - 2_{10} = 6806 V,$$

$$ra g_{\#} (0+8)/4 = (2/4.3) \gg;$$

$$re = \# , op(-vs0) = 0. \% \% ah$$

$$(a) Newsoten. \& T(@) > 1(02), \gg A that$$

$$7/, -7(@) - \# , - znc.$$

---


$$2s] a - (s-00\% - 10\% +$$

$$(a) 1a=0 \parallel aA - (wA/0)y 22. 2tlule, 4hobo,$$

$$ezo0-60 (818700- 24a1 > DY, = 2le \gg V;$$

$$@ = 4\% / a - 2 / 0.4 = 60 5-$$

$$(') 5 - 0 + 18 - 18 u, @ - 1 \& 0.0s = 1560 -$$

$$(a) AV\% - (\%av) - (so/z3) = 5i. 6, @ - 546/0.12z$$

$$= N7 -$$

2.54

$$(a) V_{BE1} = (26 \text{ mV}) \ln \frac{(6 - 0.7)/10^4}{2 \times 10^{-15}} \cong 684 \text{ mV}$$

$$V_{BE2} = 0.026 \ln \frac{0.684 - V_{BE2}}{10^3 \times 2 \times 10^{-15}}; \text{ start out with } V_{BE2} = 0.6 \text{ V.}$$

$$V_{BE2} = 0.026 \ln \frac{0.684 - 0.6}{2 \times 10^{-12}} = 0.636 \text{ V}$$

$$V_{BE2} = 0.026 \ln \frac{0.684 - 0.636}{2 \times 10^{-12}} = 0.620 \text{ V}$$

Iterate further, and end with  $V_{BE2} = 626 \text{ mV}$ .

$$I_{C2} = (0.684 - 0.626)/10^3 \cong 58 \mu\text{A}.$$

$$(c) \text{ With } V_{CC} = 6 \text{ V, } I_{C1} = (6 - 0.684)/10 = 0.5316;$$


$$(1/2)I_{C1} = 0.5316/2 = 0.2658; \text{ Rule of Thumb:}$$

$$V_{BE1} = 684 - 18 = 0.666 \text{ V; } V_{CC} = 0.666 + 10 \times 0.2658 = 3.324 \text{ V. Reiterate as before, and find}$$

$$V_{BE2} = 0.026 \ln \frac{0.666 - V_{BE2}}{2 \times 10^{-12}} \Rightarrow V_{BE2} = 620 \text{ mV} \Rightarrow$$

$I_{C2} = (0.666 - 0.620)/10^3 = 46 \mu\text{A}$ . While  $I_{C1}$  has dropped to  $\frac{1}{2}$  its initial value,  $I_{C2}$  has dropped from  $58 \mu\text{A}$  to  $46 \mu\text{A}$ . Not  $\frac{1}{2}$ , as  $I_{C2}$  is not linearly proportional to  $I_{C1}$ .

[S]

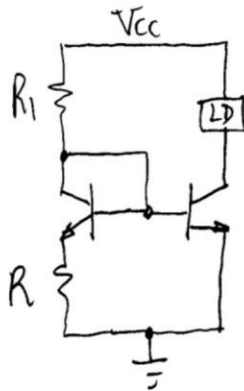

$$V_{e1} = 0.7 \text{ V}$$

$$I_{C1} = 0.5 \text{ mA} > I_{E1} = 0.7 \text{ mA}$$

$$I_{C2} = 0.5 \text{ mA} = V_{e2} = 0.7 \text{ V} + I_{R1}$$

$$\therefore I_{R1} = 0.5 \text{ mA} - 0.7 \text{ mA} = -0.2 \text{ mA}$$

$$R_1 = \frac{V_{CC} - V_{e1}}{I_{R1}} = \frac{5 \text{ V} - 0.7 \text{ V}}{-0.2 \text{ mA}} = -21.5 \text{ k}\Omega$$

( $I_{C1} = 0.5 \text{ mA} \Rightarrow I_{E1} = 0.7 \text{ mA}$ ,  $V_{e1} = 0.7 \text{ V}$ ,  $I_{C2} = 0.5 \text{ mA}$ ,  $V_{e2} = 0.7 \text{ V} + I_{R1}$ )  
 $I_{R1} = 0.5 \text{ mA} - 0.7 \text{ mA} = -0.2 \text{ mA}$   
 $R_1 = \frac{5 \text{ V} - 0.7 \text{ V}}{-0.2 \text{ mA}} = -21.5 \text{ k}\Omega$   
**Thao** le «l-al Jato»!

[ ]

$$\text{a) } \left[ \frac{V_{C1} - V_{E1}}{I_{R1}} \right] = \frac{5 \text{ V} - 0.7 \text{ V}}{0.5 \text{ mA} - 0.7 \text{ mA}} = -21.5 \text{ k}\Omega$$

$$\text{b) } R_2 = \frac{V_{CC} - V_{E1}}{I_{R2}} = \frac{5 \text{ V} - 0.7 \text{ V}}{0.5 \text{ mA} - 0.7 \text{ mA}} = -21.5 \text{ k}\Omega$$

$$K = \frac{V_{C1} - V_{E1}}{I_{R1}} = \frac{5 \text{ V} - 0.7 \text{ V}}{0.5 \text{ mA} - 0.7 \text{ mA}} = -21.5 \text{ k}\Omega$$

(b) **A owes** 2n V doeneao  $V_C$  as  $V_{E1}$ ,  $V_{E2}$

$$V_{C1} = 5 \text{ V}, V_{E1} = 0.7 \text{ V}, V_{C2} = 5 \text{ V}, V_{E2} = 0.7 \text{ V} + I_{R1}$$

$V_{C1} = 5 \text{ V}, V_{E1} = 0.7 \text{ V}$

$$I_{C1} = 0.5 \text{ mA}, I_{E1} = 0.7 \text{ mA}, I_{C2} = 0.5 \text{ mA}, I_{E2} = 0.7 \text{ mA} + I_{R1}$$

$$K = \frac{V_{C1} - V_{E1}}{I_{R1}} = \frac{5 \text{ V} - 0.7 \text{ V}}{0.5 \text{ mA} - 0.7 \text{ mA}} = -21.5 \text{ k}\Omega$$

$$\therefore R_1 = 21.5 \text{ k}\Omega$$







ass

$$@) 1\%7 \quad 74 \overset{to-0}{i} s. = 73, I + 1.07\%A,$$

$$IVg - 3713210? = 0.4IV$$

$$Ve - V_+ V_{ee}[\gg) = 0.24I + 0.7 = 0.41 V$$

$$= -10 + 71.07 - -82 V.$$

$$M_{r1} = \frac{1.0I}{Z/G} = 27n \quad \left( \overset{pr}{V} = \frac{7.44}{5} \overset{0}{0} \overset{0}{0} - \frac{44}{2} kt. \right)$$

$$\frac{K_{\overset{3}{\underset{0}{\text{do}}}} - 33/3.55 - 2 \approx \llcorner = 47/45.5 = 4.20 W$$

$$g, \quad \frac{32}{3+3.2} \quad (235i) \cdot \frac{12}{Zn2} \quad \text{--- } I' \quad vW,$$

$$e) \overset{41}{V} - V_+, = 0. + m, 5, ( ) ob$$

$$= 0 \cdot V + (k.57 ml) \text{ coot};$$

$$-W + 0. = - \bullet uzv - 121 (5av) q t;$$


$$\overset{v}{v} = -4.82V + (0.05 V) 0 \gg (e - 180);$$

$$e = 0 + (.60sv) c (t - 180^\circ);$$

$$= 0, 2V + 0,$$



S»

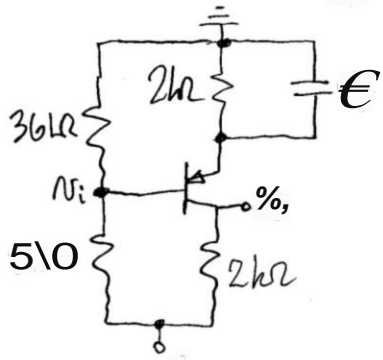

@  $V_{\%} = \frac{2e^{-4}}{3\%+51!} = 3.12V$

$s = \frac{\%}{51} = 2n$

$T_{aC} = \frac{1}{p} \frac{12-0}{21k1512} = 1. u, A$

$\theta, \sim > 208k, - 310$

-aw @v-  $\%//s//28-25\backslash3, R.=2/13-2610,$

$eh = \frac{\%}{10} = -2.9\% \cdot 0,01855 = -133 L.$

€)  $-e Re/(e.+)- 18.5+21g0/1915 1600.$

$- 1/( <60 \times 10^?) 2 J. le Cc=10,F.$


[z@] ;V, +, a].  $- t0-. 1c+681z/21+07 >$

$e=2.08\%n Ic=2.07\%A \} = 1/(2.\% n), Yr=$

$15n, 1 \cdot z 48 M, R//. = 3./48 3.\% 2$

$\ll - \int Rr+(a) \cdot e_{8+3.1} - z 2n$   
 $"l jg(@d.) " + 3. @/. 6$

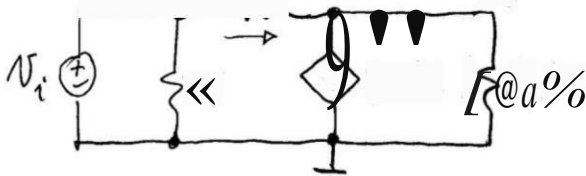$= oh[: \{ ] e \ll f_{t. \#4} \cdot \ll sr$



$\frac{v_i}{ne} e = \pm \frac{\bullet}{\bullet}$

@%. U - o"" @el.

$e(\#e - \cdot (\# \% > i. n.$

$\#.: - \% - \#k)(eel&dee) = -(kn.ka)(@m L/) \} \cdot zn \bullet$




[26] @)  $I_{\phi} = 1 \mu A, I_D = 10 \mu A, I_{D0} = 10 \mu A, \beta = 100$

$V_{GS} = V_{DS} = V_{DD} - I_D R_D = 10V - 10 \mu A \cdot 1M = 10V - 10V = 0V$   
 $V_{GS} = 0V, V_{DS} = 0V$

5M:

[F

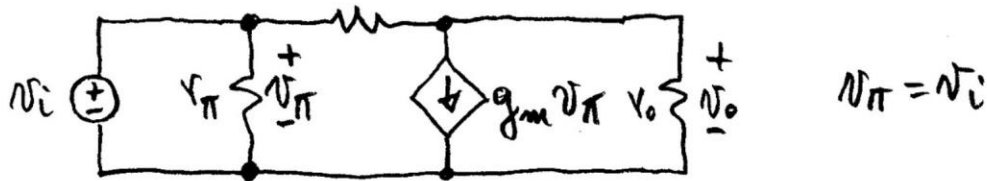

CL:  $V_{GS} = \frac{V_{DD} - I_D R_D}{1 + \beta R_D} = \frac{10V - 10 \mu A \cdot 1M}{1 + 100 \cdot 1M} = \frac{10V - 10V}{1 + 100M} = 0V$

$V_{DS} = V_{DD} - I_D R_D = 10V - 10 \mu A \cdot 1M = 10V - 10V = 0V$


$V_{GS} = 0V, V_{DS} = 0V$

(b)  $V_{GS} = 0V, V_{DS} = 0V$

$V_{GS} = 0V, V_{DS} = 0V$

$V_{GS} = 0V, V_{DS} = 0V$

2.62

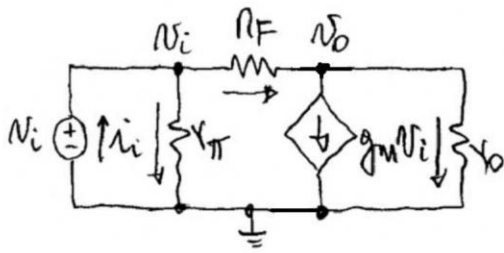(a)  $I_C = 1 \text{ mA} \Rightarrow g_m = 1/(26 \Omega)$ ,  $r_{\pi} = 2.6 \text{ k}\Omega$ ,  $r_o = 100 \text{ k}\Omega$ .

$$\text{KCL: } i_i = \frac{v_i}{r_{\pi}} + \frac{v_i - v_o}{R_F} = \frac{v_i}{r_{\pi} // R_F} - \frac{v_o}{R_F}$$

$$\text{KCL: } \frac{v_i - v_o}{R_F} = g_m v_i + \frac{v_o}{r_o} \Rightarrow$$

$$\frac{1 - g_m R_F}{R_F} v_i = \frac{v_o}{R_F // r_o} \Rightarrow$$

$$v_o = \frac{1 - g_m R_F}{R_F} \frac{R_F // r_o}{R_F // r_o} v_i = \frac{1 - g_m R_F}{1 + R_F / r_o} v_i \Rightarrow i_i = \frac{v_i}{r_{\pi} // R_F} - \frac{1 - g_m R_F}{R_F (1 + R_F / r_o)} v_i$$


$$R_i = \frac{v_i}{i_i} = r_{\pi} // R_F // \frac{R_F (1 + R_F / r_o)}{g_m R_F - 1} = 2.6 // 100 // \frac{100 (1 + 100 / 100)}{100 / 0.026 - 1} \approx 52 \Omega.$$

If  $R_L = 100 \text{ k}\Omega$ , replace  $r_o$  with  $r_o // R_L = 100 // 100 = 50 \text{ k}\Omega$ . Then,

$$R_i = 2.6 // 100 // \frac{100 (1 + 100 / 50)}{100 / 0.026 - 1} \approx 76 \Omega. R_i \text{ is dominated by}$$

the third term, roughly representing  $R_F$  divided by the gain  $|v_o/v_i|$  (Miller effect). Loading the amplifier reduces the gain and thus increases  $R_i$ .

(b)

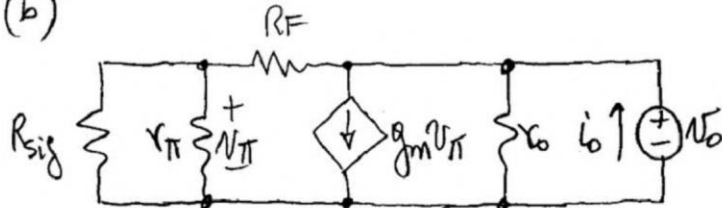

$$i_o = \frac{v_o}{r_o} + \frac{v_o}{R_F + (R_{sig} // r_{\pi})} + g_m \frac{R_{sig} // r_{\pi}}{R_F + (R_{sig} // r_{\pi})} v_o = v_o \left[ \frac{1}{r_o} + \frac{1 + g_m (R_{sig} // r_{\pi})}{R_F + (R_{sig} // r_{\pi})} \right]$$


$$R_o = \frac{v_o}{i_o} = r_o // \frac{R_F + (R_{sig} // r_{\pi})}{1 + g_m (R_{sig} // r_{\pi})}. R_o (R_{sig} = 0) = r_o // R_F = 50 \text{ k}\Omega.$$

$$R_o (R_{sig} = 1 \text{ k}\Omega) = 100 // \frac{100 + 1 // 2.6}{1 + (1 // 2.6) / 0.026} \approx 3.4 \text{ k}\Omega$$

With  $R_{sig} \neq 0$ ,  $v_{\pi} \neq 0$  and  $g_m v_{\pi} \neq 0$ , so  $i_o$  increases, reducing  $R_o$ . In the limit  $R_{sig} \rightarrow \infty$ , we get  $R_o \rightarrow 1 \text{ k}\Omega$ .

2.63

[, Au]: 2. «el>

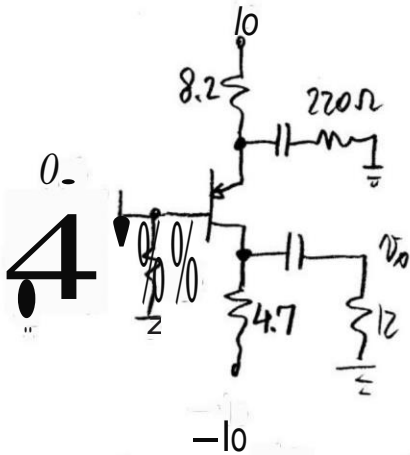

$$Te = \frac{10 - 97}{33 + 2 \cdot 8.2} \approx 724$$

$$C = 253572 = 40\% A$$

$$7m = \frac{1}{i_T} \approx 75.7$$

$$Gr = 2523,8218 k$$

$$-(a/n = 3/f + (1as6)(3.2/0)) - 1s.9 \ln$$

Kz802kl

$$e^{158} \left[ \frac{L^{3.8}}{1 + (\sqrt{527} \cdot g)^2} \right] \cdot 7^2$$

[264] (@)  $\approx 105 \cdot \frac{10^{-07}}{100 + 2\%} \cdot g \cdot 7 \mu, \quad 0^{\rightarrow} = 07/2\% =$

1/(72),  $\approx 257 + .\phi \text{ kn.}$

«; - (@0  $L/Rs = 10/[4.6 + 1\%(s/0.)] - .4w, t = 0l.$

$\frac{e}{k., (v_{S-v}) @ ?} - \frac{10 \cdot e^{137}}{1 + 19.15} F74 / .$

6)  $oa + |sa//\langle, - 00 + [sol/31 + \{ \$; )]$

$= 88 - c > \sqrt{0.a \& 88702} - 1 \& F.$

Ve 20F.

e tie , th «  $\langle \rangle \cdot hp \gg t\% \# : - \# ; t ; -- 0 \ll \sqrt{v.}$

vs] @)Mee - .0ls- lo, 5- [75//o+15]1=3%.  
Tc-00<sub>0+101x22</sub> 2.01 oal, w.- m, a) - 200.

he-t/fat +o@a]:- kn, .7 27 In



A/- 'ht toon?7=- 1. //

, tell@vu. 5:1- son  
> i/(c?«zo)- «5F ve Cs=19F.  
6<sup>5i</sup>5-, kt- -, 4the-!





Z <<

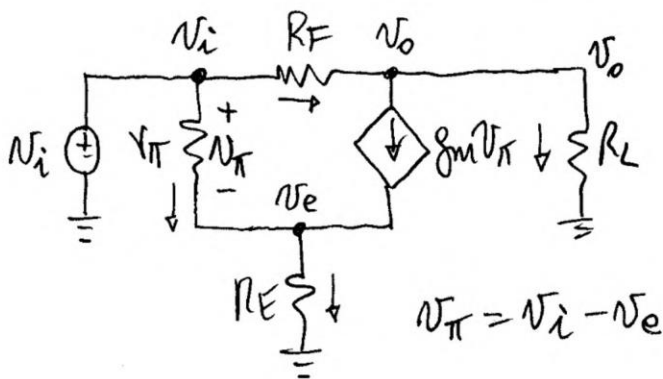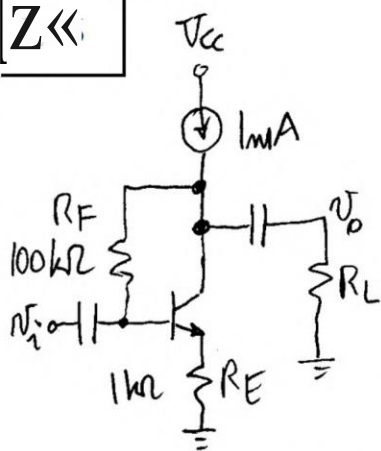

$$I_c = \alpha I_E = \frac{150}{151} I \approx 1 \text{ mA}, \quad g_m = \frac{1}{26.2 \Omega}, \quad r_\pi = 39.3 \text{ k}\Omega.$$

$$\text{kCL @ } v_e: \frac{v_i - v_e}{r_\pi} + g_m (v_i - v_e) = \frac{v_e}{R_E} \Rightarrow v_e = \frac{1}{1 + r_e/R_E} v_i$$

$$\text{kCL @ } v_o: \frac{v_i - v_o}{R_F} = g_m (v_i - v_e) + \frac{v_o}{R_L} \Rightarrow$$

$$v_i \left( \frac{1}{R_F} - g_m + \frac{g_m}{1 + r_e/R_E} \right) = v_o \left( \frac{1}{R_F} + \frac{1}{R_L} \right) = \frac{v_o}{R_F/R_L}$$

$$\frac{v_o}{v_i} = \frac{R_F R_L}{R_F + R_L} \frac{1}{R_F} \left[ 1 - g_m R_F \left( 1 - \frac{1}{1 + r_e/R_E} \right) \right] = \frac{R_L}{R_F + R_L} \left[ 1 - g_m R_F \frac{r_e}{R_E + r_e} \right]$$

But,  $g_m r_e \approx 1$ , so

$$\frac{v_o}{v_i} = \frac{1}{1 + R_F/R_L} \left( 1 - \frac{R_F}{R_E + r_e} \right) = \frac{1}{1 + 100/100} \left( 1 - \frac{100}{1 + 0.026} \right) \approx -48 \text{ V/V.}$$

For  $R_E \gg r_e$ , we can approximate

$$\frac{v_o}{v_i} \rightarrow \left( 1 - \frac{R_F}{R_E} \right) \frac{1}{1 + R_F/R_L} = -\frac{99}{2} \text{ V/V.}$$

2.67

$$(a) R_i = r_{\pi 1} + (\beta_{01} + 1)(R_E // r_{e2}) \cong r_{\pi 1} + (\beta_{01} + 1)r_{e2} = 2r_{\pi 1};$$

$$R_c = r_{o1} [1 + g_{m1}(r_{\pi 1} // R_E // r_{e2})] \cong r_{o1} [1 + g_{m1}r_{e2}] \cong 2r_{o1};$$

$$R_o = R_c // R_L \cong R_c; \quad \frac{V_o}{V_{sig}} = - \frac{g_{m1} R_o}{1 + g_{m1}(R_E // r_{e2})} \cong - \frac{g_{m1} R_o}{2}.$$

$$(b) I_{C1} \cong I_{E1} = \frac{1}{2} \frac{12 - 0.7}{7.5} \cong 0.75 \text{ mA}$$

$$g_m = \frac{0.75}{26} = \frac{1}{34.7 \Omega}, \quad r_{o1} = \frac{100}{0.75} = 133 \text{ k}\Omega; \quad r_{\pi 1} = 200 \times 34.7 = 6.9 \text{ k}\Omega$$

$$R_i \cong 2r_{\pi 1} = 13.8 \text{ k}\Omega; \quad R_c \cong 2 \times 133 = 267 \text{ k}\Omega; \quad R_o = R_c // R_L = 267 // 10 = 9.64 \text{ k}\Omega; \quad \frac{V_o}{V_{sig}} = - \frac{1}{2} \frac{9640}{34.7} \cong -140 \text{ V/V}.$$

$$268] \frac{V_0}{Ois} = \frac{1}{1 + \frac{R + \pi}{(3+0)(1K_0)}} \stackrel{1/2}{=} \frac{1}{1 + \frac{R_{sig} + \pi}{(\beta_0 + 1)R_L}}$$

Woe<sub>n</sub> << Oe @ \$ r >> K<sub>-</sub>.

$$0.853 = \frac{L \cdot Dk}{(+)700} = \frac{1}{1 + e/00} \quad Y_{\phi} = 5/752$$

> I<sub>φ</sub> / % = 26/5'7 0.5 uh.

$$0.1!&- \frac{k't}{-(@)_L} = \frac{1}{1 + \frac{10^4}{(\%+) \%0}} \cdot fe^{-4\phi 33.2, 51} + I_{30}$$

7(- 150 , Y« = 1551.7 = 775 -

#ij, ass'n a- 08W VW.  
T - 75ix-zoo 5


$$z @ | e \# k t, (w) = - . v, k w - c / = 2.8 \bullet$$

$$\frac{1}{7} \frac{1-0}{a} \downarrow 7 \text{ mA} ; r_s = 26 \bullet$$

$$0.5 \times 13.2 - 1.65 \text{ nI}, w - 80 / .7 = 10 \bullet W I = w$$

$$- \delta \text{ all } [ \ll e \{ + \} (e e 1, k.) . / \text{ fust a } (1 e k) = k$$
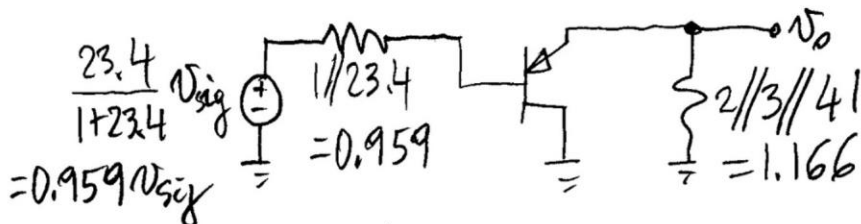
$$t - v \text{ ft } \ddot{e}'' - ] \# \text{ Morr } \# - a o a e$$



$$\frac{v_o}{v_{sig}} = 0.959 \frac{1}{1 + \frac{1.65 + 0.959}{126 \times 1.166}} = 0.942 \text{ V/V.}$$


2.70

$$(a) I_C = 100 \frac{6 - 0.7}{20 + 101 \times 3} = 1.64 \text{ mA}, r_e = 15.7 \Omega,$$

$$r_{\pi} \approx 1.6 \text{ k}\Omega. R_i = 20 \parallel (1.6 + 101 \times 3) \approx 19 \text{ k}\Omega$$

$$R_o = 3,000 \parallel [15.7 + (10,000 \parallel 20,000) / 101] \approx 80 \Omega.$$

Thévenize:

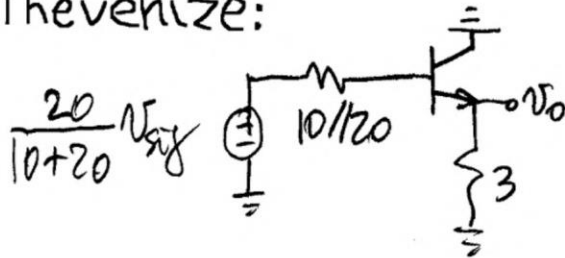

$$\frac{V_o}{\frac{2}{3} V_{sig}} = \frac{1}{1 + \frac{1.6 + (10 \parallel 20)}{101 \times 3}}$$

$$\frac{V_o}{V_{sig}} = 0.649 \text{ V/V}$$

(b) With  $C_2$  in place, the upper  $10\text{-k}\Omega$  resistance is placed in parallel with  $r_{\pi}$ , giving  $r_{\pi(eq)} = 10 \parallel 1.6 \approx 1.4 \text{ k}\Omega$ ; the lower  $10\text{-k}\Omega$  resistance is placed in parallel with  $R_E$ , giving  $R_{E(eq)} = 10 \parallel 3 = 2.3 \text{ k}\Omega$ .

We now have

$$R_i = r_{\pi(eq)} + (\beta_0 + 1) R_{E(eq)} = 1.4 + 101 \times 2.3 = 234 \text{ k}\Omega$$

$$R_o = R_{E(eq)} \parallel \left( r_e + \frac{R_{sig}}{\beta_0 + 1} \right) = 2,300 \parallel \left( 15.7 + \frac{10,000}{101} \right) = 110 \Omega$$

$$\frac{V_o}{V_{sig}} = \frac{1}{1 + \frac{r_{\pi(eq)} + R_{sig}}{(\beta_0 + 1) R_{E(eq)}}} = \frac{1}{1 + \frac{1.4 + 10}{101 \times 2.3}} = 0.953 \text{ V.}$$

Bootstrapping increases  $R_i$  significantly, thus reducing input loading and making gain closer to unity.

$$[2n_{Jr}, -(s-05)/4. - \cdot \int mA, : 2\% n = / \% n;$$

$$= 115 / = 16 k9; - 10 = 3 \cdot w2$$

$$\bullet \cdot \underline{Lo} n - \underline{75} (0s) a \underline{l}$$

$$e = (\% .8 \gg V) 0, -0, e \underline{l} \phi = e /$$

$$Ce + (@ // .) \underline{0,020} + (4 \underline{75})$$

n ~

$$l., Q | -.5) - IA) te? wb$$

$$(sad \epsilon \} \underline{-} [ \underline{-} @ e / a$$

$$\underline{\ll 59a [11 @ 300 / 1) // .]} = 6 mr -$$

$$[FI 1a - \$ - ta;$$

$$e = Ye = 08 (2 / 1.1) - 22.8 Q;$$

$$m = Yz - 100 (26 / 1.13)^{e2} = 2.3 \underline{u}$$

$$8 = fr + (0a+) (( 'el / Ra), (= z + (pa+) (@ / ht,)$$

$$\& - \& el / Re, \ll e \underline{-} \text{£gyW}$$

$$K \underline{t} \underline{23} + 10 \underline{\ll} (10 // 0) - (7\% \underline{ML}$$

$$\underline{K} - \underline{2.3} + \underline{10} \underline{\ll} (10 // \% 70) \underline{1mM} \underline{c} \underline{x}$$

$$\& - 22s + \underline{4}; \underline{vn}, 0. - \underline{//} 2z0352.$$

$$0 \quad V_0 \quad e, \quad R_{up} \quad fRe \quad 2000 \quad 1e000$$


$$0e \quad sr \quad , \quad \underline{TR}^c \quad \underline{er+fe1} \quad 23+20\phi e \quad 23 + 0w00$$

$$0.4\% 5 \underline{Vly} \bullet$$






2.73

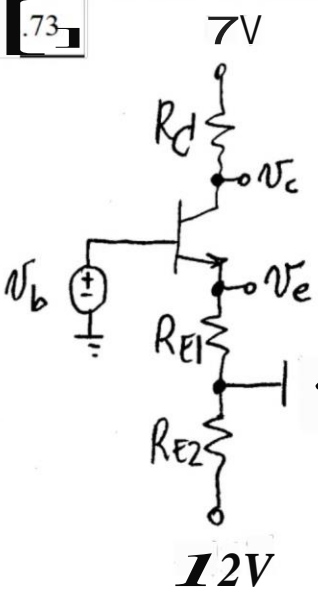

1W.  $I=1A$ ,  $V=V$ .  
 $=R=GM$  (ee 4.2M., 5%)  
 We kootit  $cefo \approx 4V$ ,  
 to t a  $UeL, z-1 4V$   
 $fer-f=6.2$   
 $wu Lc l mA, z$   
 nod.  $e fe - (r-0) A,$   
 $Ke=11.3-2=5.10, 5\%$

8-  $eL // (et,) - s. / (6a+0o0) - 2. & -$   
 $C > \frac{2r28 \neq 10^3}{y \cdot 0} t - 5aF. Uk - tuF.$

2.74

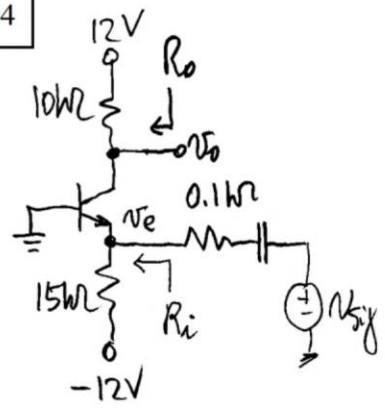

$I_C \approx I_E = \frac{12-0.7}{15} = 0.753 mA$   
 $r_e = \frac{26}{0.753} \approx 35 \Omega$ .  $R_o \approx 10k \Omega$ .  
 $R_i = 35 // (15k) \approx 35 \Omega$ .  
 $v_{ce} = \frac{0.035}{0.035+0.1} v_{sig} = 0.26 v_{sig}$

$v_o = g_m v_e R_o = \frac{1}{35} (0.26 v_{sig}) 10,000 = 74 v_{sig}$ .  $v_o/v_{sig} = 74 V/V$ .

[r] p, -, £- . SW (we . W;

$$e_{\text{eff}} = 10. R = 2.7 - 25 \text{ (we 2.4)}$$

$$|g| = \frac{R_1}{x + @ - F5} - \frac{2400}{r + (@CC7@)} = \frac{I_c}{7H_{00}} \cdot /p \rightarrow -227 \rightarrow$$

cha, 'k:  $\pm 0 = 28(n \ 2402)$ .

2.76 (a)  $R_i = R_1 // R_{e1}, R_{e1} = r_{e1} + \frac{r_{e2} // R_2}{\beta_{01} + 1} \cong r_{e1}$ ;

$$r_{e1} = \frac{V_T}{I_{C1}} \cong \frac{26}{10/10} = 26 \Omega; R_i = 10,000 // 26 \cong 26 \Omega.$$

$$R_o \cong r_{o1} \left[ 1 + g_{m1} (R_{sig} // R_1 // r_{\pi 1}) \right] = \frac{80}{1} \left[ 1 + \frac{1 // 10 // (150 \times 0.026)}{0.026} \right]$$

$$\cong 2.35 \text{ M}\Omega. v_i = \frac{R_i}{R_{sig} + R_i} v_{sig} = \frac{26}{1000 + 26} v_{sig} = \frac{v_{sig}}{39.5}.$$

$$i_o = g_m v_i = \frac{1}{26} \frac{v_{sig}}{39.5} = \frac{v_{sig}}{1026 \Omega}.$$

(b)  $v_o = (R_L // R_o) i_o \cong R_L i_o = \frac{5000}{1026} v_{sig} \Rightarrow \frac{v_o}{v_{sig}} = 4.87 \text{ V/V}.$

(c) As long as  $R_{sig} \gg R_i$  and  $R_L \ll R_o$ , we have

$$v_o = R_L i_o = R_L v_i \cong R_L (v_{sig} / R_{sig}) \Rightarrow v_o / v_{sig} \cong R_L / R_{sig} = 5 \text{ V/V}.$$